

# Tips on High Speed Digital Design


by

Lakshmanan B

# High Speed Scenario

- Effect of passive circuit elements - wires, IC packages, PCBs.
  - Signal propagation (Reflection & ringing)
  - Interaction between signals (crosstalk)
  - Interaction with natural world (EMI)

# Knee Frequency

 

**Figure 1.1** Expected spectral power density of a random digital waveform.


$$F_{knee} = \frac{1}{2T_r}$$

- Not a substitute for Fourier analysis
- Precise risetime measurement
- EM emissions depend upon spectral behavior well above  $F_{knee}$

# Time and Distance

- Propagation delay is proportional to the square root of the dielectric constant.
- The propagation delay of signals traveling in air is 85 ps/in.
- Outer-layer PCB traces are always faster than inner traces.

# Lumped Vs Distributed systems

 

**Figure 1.3** Snapshots in time of the electric potential on distributed and lumped transmission lines.

$$l = \frac{T_r}{D}$$

For PCB traces, point to point wiring and bus structures,

- length  $< l/6$  - Lumped
- length  $> l/6$  - Distributed

# High speed properties of Logic Gates


- Power
  - Speed
  - Packaging
1. Standard packaging - money, flexibility, limits number of pins and gates per package, partitioning, power and speed constraints
  2. Max power dissipation per package - package, cooling properties
  3. Speed Vs Power

# Power

- Input Power
- Internal dissipation
- Drive Circuit dissipation
- Output power

Quiescent and Active components


# Power in Logic Gates - Categories

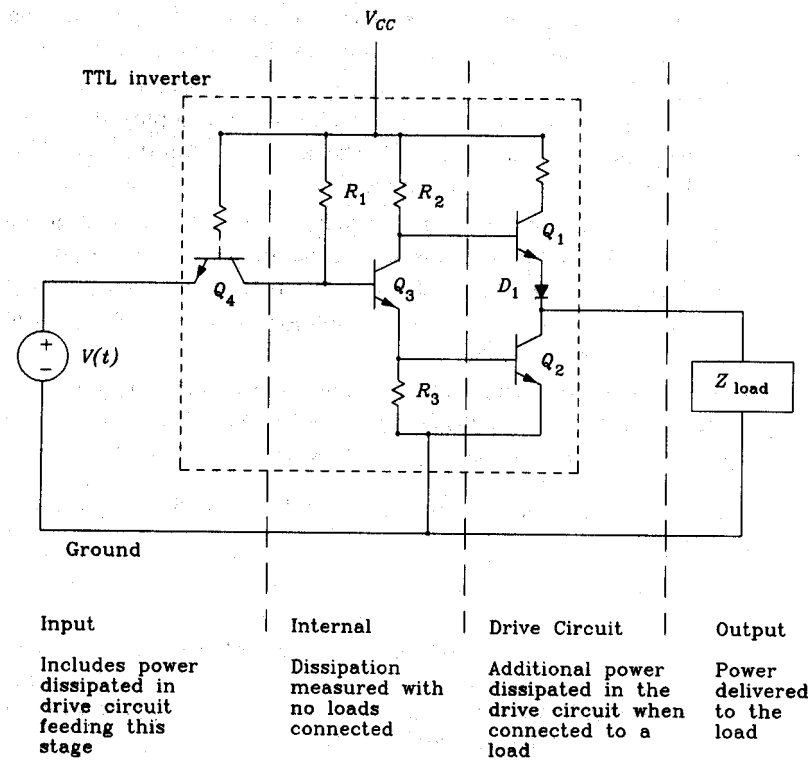

**Figure 2.1** Categories of power dissipation in and around a logic device.



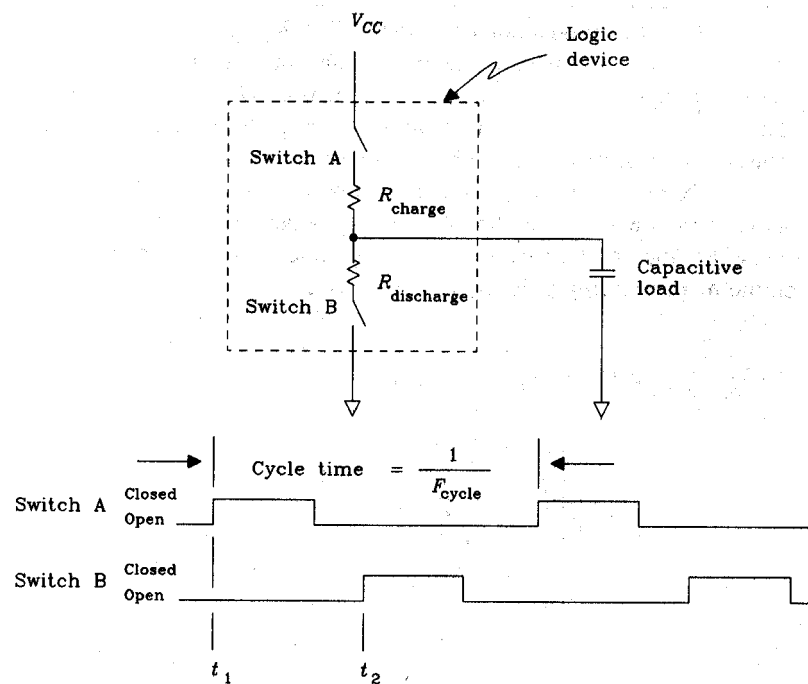
# Active power dissipation when driving a Capacitive load



$$P_{\text{active}} = F C V_{CC}^2$$

 
# Active Power - Overlapping Bias currents



Less in Schottky

CMOS, TTL, ECL
 
# DC consumption of Signetics 74HC00 family




# Input Characteristics of Logic Families

**TABLE 2.1 INPUT CHARACTERISTICS**

	74HCT00	74AS00	10H101	10G001
$I_{in HI}$ (mA)	0	+0.020	+0.425	+0.400
$I_{in LO}$ (mA)	0	-0.500	+0.0005	-0.100
$P_{quiescent}$ (mW)	0	1.3	1.1	1.3
$C_{in}$ (pF)	3.5	3	3	1.5
$\Delta V_{in}$ (V)	5.0	3.7	1.0	1.5
$P_{active}$ (mW)				
$F = 1$ MHz	0.09	0.04	0.003	0.003
$F = 10$ MHz	0.9	0.4	0.03	0.03
$F = 100$ MHz			0.3	0.3
$F = 1000$ MHz				3.0

# Internal Power dissipation

 


$$K_{active} = \frac{P_{total} - P_{quiescent}}{F}$$

# Drive Circuit Dissipation



- Totem pole
- Emitter follower
- Open Collector
- Current Source
 
# Quiescent Power - Totem-pole output circuit




$$P_{quies} = \frac{0.4I_{Sink} + 1.0I_{Source}}{2}$$
  
# Quiescent Power in CMOS Totem-pole output circuit






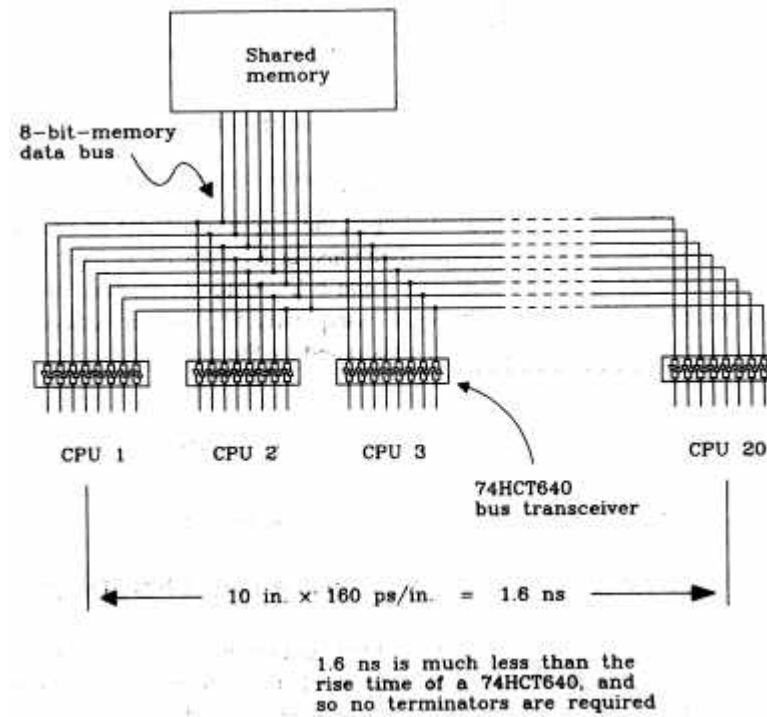
# Active Power in Totem-pole output circuit


 
# Rise and Fall times in Emitter follower circuit



 
Rise time is determined by the equivalent emitter series resistance  $R_E$  and the capacitive load  $C$




Fall time depends on the pull down resistor, the capacitor  $C$  and the value of  $V_T$  compared to  $V_{LO}$

Signal falls towards  $V_T$  but is caught by  $Q_1$  and held at  $V_{LO}$

# BTL Output

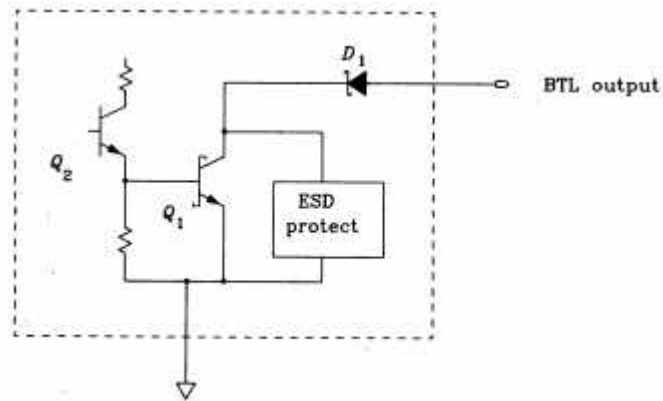

# Current source drivers

 


# Output Dissipation

- Power supply - Terminating resistors, pull-down resistors, or other bias resistors

# Speed


- Effects of sudden change in voltage,  $dV/dt$
- Effects of sudden change in current,  $dI/dt$
 
# Output switching time $V_s$ Propagation delay



# Max current slew rate Vs Voltage


## Rise time

 

$$I(t) = \underbrace{\frac{V(t)}{R}}_{\text{Current through resistor}} + \underbrace{C \left( \frac{dV(t)}{dt} \right)}_{\text{Current through capacitor}}$$


Rate of  
change of  
current
 
$$\frac{dI(t)}{dt} = \frac{1}{R} \left( \frac{dV(t)}{dt} \right) + C \left( \frac{d^2 V(t)}{dt^2} \right)$$






# DC Voltage margins for 10KH ECL

 


# Ground Bounce - Lead Inductance

 


$$V_{GND} = L_{GND} \frac{d}{dt} (I_{discharge})$$

# Ground bounce an example

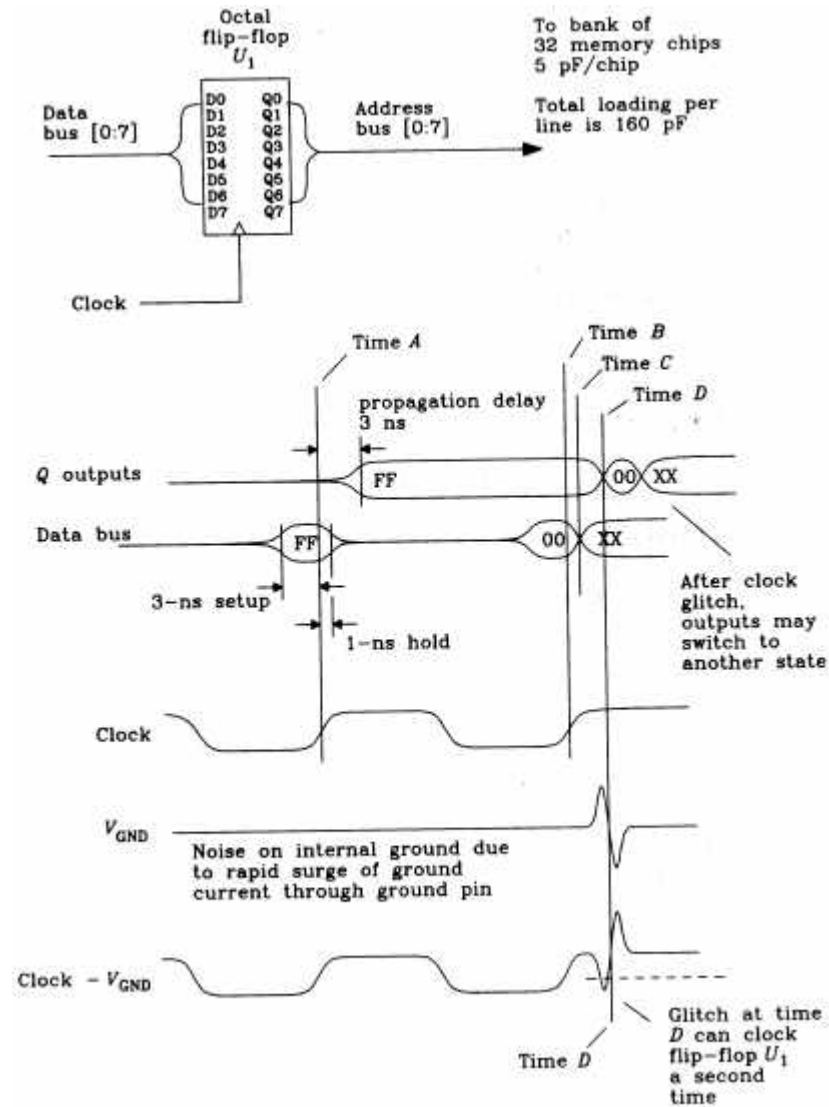


# Packages


## Wire Bond

 


## Tape Automated Bonding

 


## Flip-Chip

 

# Lead Capacitance

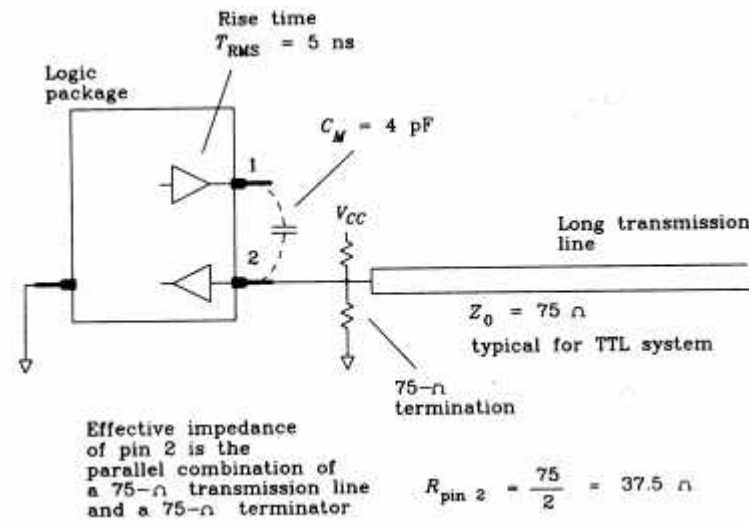
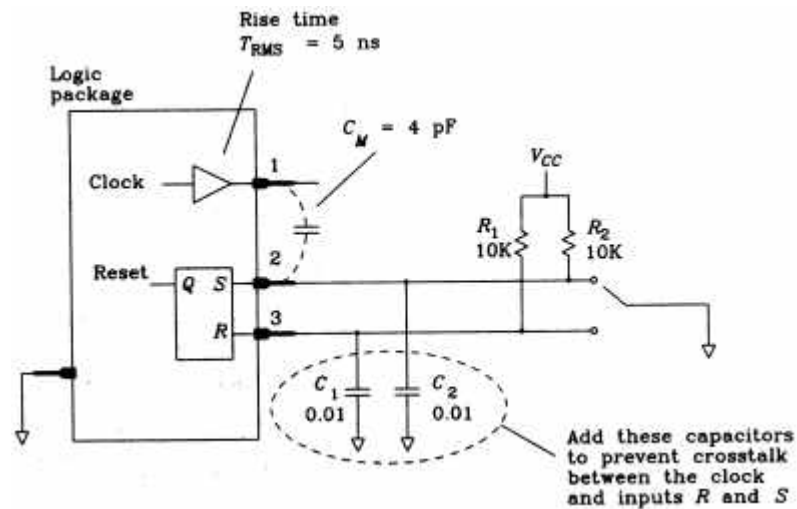
# Stray capacitance problem in a debouncing circuit




# References

- “High- Speed Digital Design - A Handbook of Black Magic”, Howard Johnson, Martin Graham, Printice Hall PTR, 1993

# HIGH-SPEED DIGITAL DESIGN

*A HANDBOOK OF BLACK MAGIC*

 

Howard Johnson  
Martin Graham