

5 Basic ideas of electricity

5.1 Electric current and source

1 Which one of the following statements about atom is **not** true ?

- A An atom is extremely small
 B An atom has a nucleus
 C An atom has electrons
 D An atom has no mass

2 What is an electric current made up of ?

- A static charges
 B moving charges
 C atoms
 D molecules


3 Electricity is a flow of

- A atoms
 B electrons
 C neutrons
 D molecules

4 The conventional current flows

- A from the positive terminal of a battery to the negative terminal of the battery
 B from the negative terminal of a battery to the positive terminal of the battery
 C in a clockwise direction
 D in an anti-clockwise direction

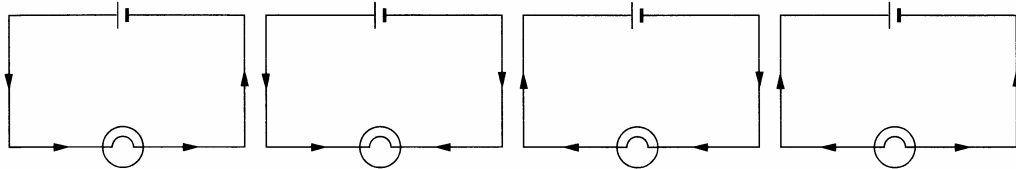5 Which one of the following circuit diagrams shows correctly the direction of flow of conventional current?



Answer: A

6 Current flowing in a copper wire is actually a flow of

- A copper atoms
 B copper ions
 C nucleus
 D electrons

7 Copper is commonly used for making electric wires because

- A it is a good conductor of electricity
 B it is a cheap metal
 C it is a heavy metal
 D it is an active metal


8 Which one of the following is a conductor of electricity ?

- A Bakelite
 B Carbon
 C Porcelain
 D Mica

9 A bicycle lamp gets its source of electricity from a

- A dry cell
 B accumulator
 C battery
 D dynamo

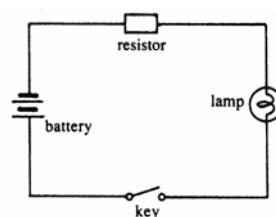10 The following figure shows an electrical circuit. The lamp lights up when switch is closed. What drives the current through the circuit ?



- A Switch
 B Cell
 C Electrons
 D Atoms


11 Answer: A

5.2 Simple electrical circuits

1 At home, electric bulbs are usually connected


- A in series **B in parallel** C to a battery D to a resistor

2 What is the symbol for resistor?

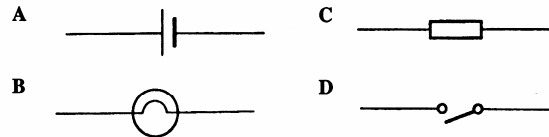

2 Answer: C

3 The correct symbol for a switch is

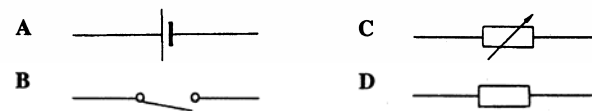


3 Answer: B

4 A series circuit has


- A no paths for the current to flow
B only one path for the current to flow
 C only two paths for the current to flow
 D one or more paths for the current to flow

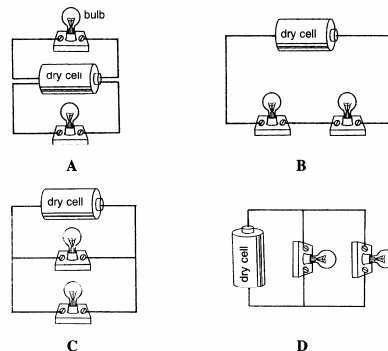5 In which of these circuits are the bulbs connected in series?




5 Answer: B

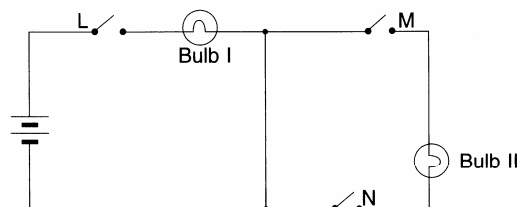6 In the circuit below which switches L, M or N must be closed for bulb 1 only to light up?



- A Switch L only** B Switch L and M C Switch L and N D Switch L, M and N

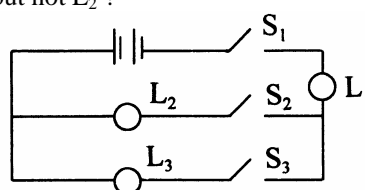
7 The diagram shows a circuit consisting of three lamps and three switches. Which of the following switches should be closed to light L_1 and L_3 but not L_2 ?




- A S_1 and S_2 only **B S_1 and S_3 only** C S_2 and S_3 only D S_1, S_2 and S_3

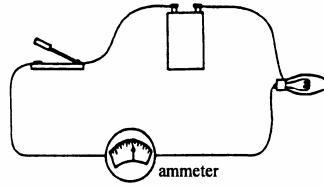5.2 Simple electrical circuits

8 An electric circuit is connected as shown in the diagram.




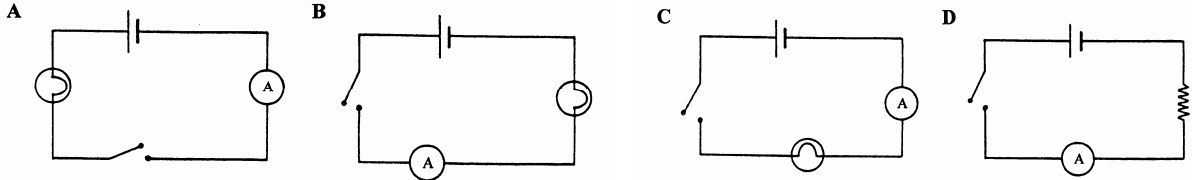Which circuit diagram shows the correct representation of the above circuit?



8 Answer: B

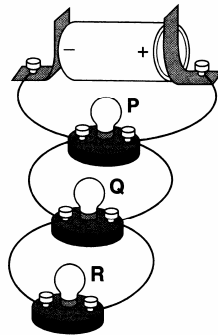
9 The diagram shows an electrical circuit (98)



If bulb P is removed, then


- A bulb Q will not light up
- B bulb R will not light up
- C both bulb Q and bulb R will not light up
- D both bulb Q and bulb R stay bright

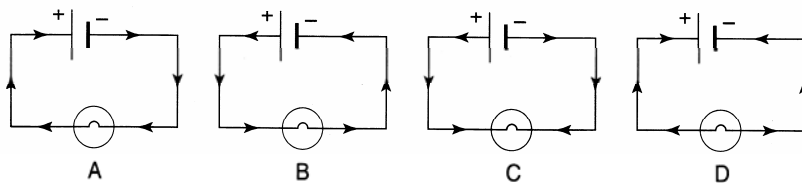10 Which of the following circuit diagrams shows the correct direction of the flow of electrons? (99)



10 Answer: A

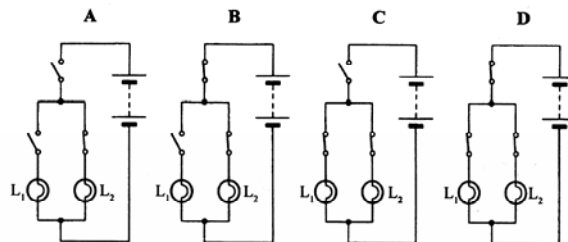11 In which of the following circuits does only lamp L₂ light?



11 Answer: B

12 Three bulbs are connected in series with a battery. One of the bulbs is removed. What would happen ?

- A The two remaining bulbs light up
- B Only one of the bulbs lights up
- C The two remaining bulbs do not light up
- D One of the bulbs is brighter than the other


13 Answer: C

14 No Answer: incomplete info

15 Answer: A

5.3 Use of ammeters and voltmeters

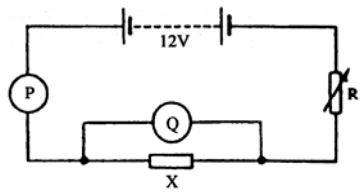Questions 1 and 2 refer to the following circuit diagram.



1 Which one is the ammeter?

- A P
- B Q
- C R
- D X


2 Which one is the voltmeter?

- A P
- B Q
- C R
- D X

3 Which one of the following shows the correct units for current, voltage and resistance?

	Current	Voltage	Resistance
A	volt	ampere	ohm
B	ohm	volt	ampere
C	volt	ohm	ampere
D	ampere	volt	ohm

4 The diagram below shows an ammeter.

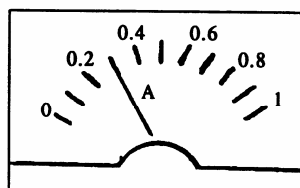


What quantity is measured using an ammeter?

- A voltage
- B current
- C resistance
- D power

5.3 Use of ammeters and voltmeters


5 The diagram below shows a voltmeter.

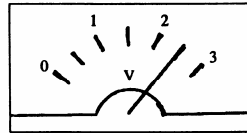

What is the reading of the voltmeter and what is the quantity measured?

	Voltmeter reading	Quantity measured
A	2.5V	current
B	2.5V	voltage
C	5.0V	current
D	5.0V	voltage

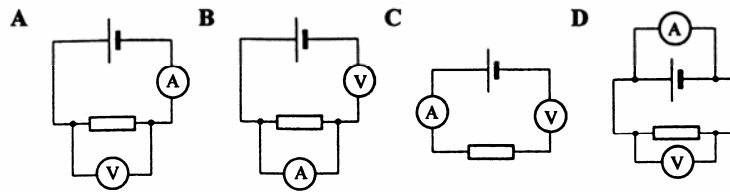6 Which circuit diagram shows the correct connection for ammeter and voltmeter?



6 Answer: A


7 To measure the current in an electrical component, an ammeter is connected

- A in parallel to the component
- B in series to the component
- C in series to the electrical source
- D in parallel to the electrical source

8 To measure the voltage across an electrical component, a voltmeter is connected


- A in parallel to the component
- B in series with the component
- C in series with the electrical source
- D in parallel to the electrical source

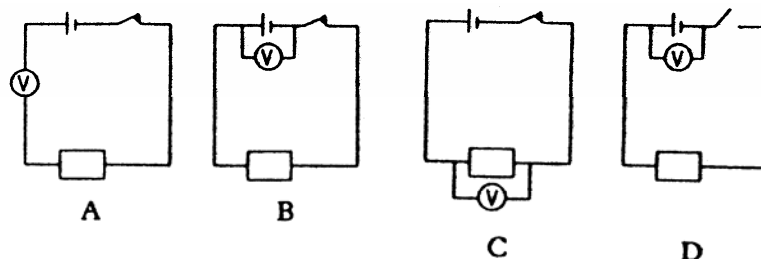9 In which one of the following circuits is the voltmeter showing the voltage of the cell ?



9 Answer: B

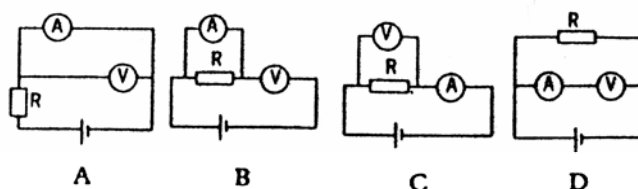10 Ahmad wants to measure the current and voltage across the resistor R. Which one of the following is the correct circuit for the above measurement?



10 Answer: C

5.3 Use of ammeters and voltmeters

11 The figure shows an ammeter scale. What is the amount of current passing through the meter?



- A 0.4A B 0.5A C 0.45A D 0.6A

12 In Brunei, electrical energy is supplied to our homes at a voltage of

- A 50V B 230V C 110V D 500V

13 Answer: D

14 Answer: A

5 Basic ideas of electricity


1 Complete the following table by drawing the appropriate circuit symbols.

(a)	(b)	(c)
Two bulbs in parallel	Three cells in series	A switch

2 Draw the appropriate circuit symbols in the following table.

(a)	(b)	(c)	(d)
An ammeter	A voltmeter	A resistor	Two bulbs in series

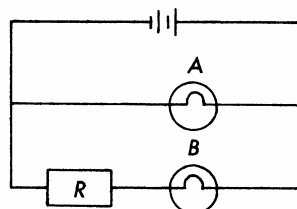3 Two identical bulbs A and B are connected as shown.



(a) Which bulb, A or B, is brighter ? Explain.


.....

(b) State the type of connection between

(i) bulb A and bulb B

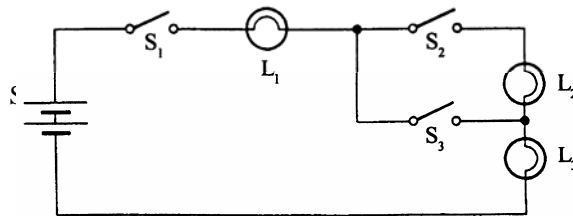(ii) resistor R and bulb B

4 The following circuit diagram shows three similar lamps, L_1, L_2, L_3 and three switches, S_1, S_2, S_3




In the following table, state which lamps, if any, will be lit for each of the following conditions

switch S_1	switch S_2	switch S_3		lamps on
closed	Open	Closed		
closed	Open	Open		
open	Closed	Closed		
closed	Closed	Open		

5 Basic ideas of electricity

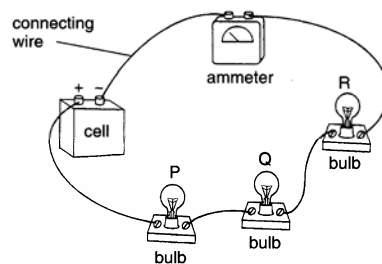5 (a) Draw a circuit diagram for the following circuit. Label the bulbs P, Q and R.



(i) How are the bulbs arranged in this circuit?

(ii) If bulb P is removed and circuit reconnected, how would this affect the brightness of bulb Q and R ?

Brightness of bulb Q

Brightness of bulb R


7

 (b) Draw a circuit diagram for the following

circuit. Label the bulbs P, Q and R.




science 2 federal test papers
 presscott pg 84Q 5b



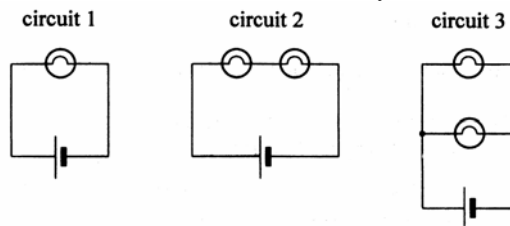- (i) How are the bulbs arranged in this circuit?
- (ii) If bulb R is removed, how would this affect the brightness of bulb Q and P ?
- Brightness of bulb Q Brightness of bulb P

5 Basic ideas of electricity

6 The following diagrams show three electrical circuits. The battery has the same voltage in each circuit.




- (a) In which circuit will the lamp or lamps be brightest?
- (b) State the type of connection of electric bulbs in
- (i) circuit 2 (ii) circuit 3
- (c) On circuit 3, show by writing an X , where a switch could be placed to switch both lamps on and off at the same time.

7 (a) What are the readings on the following meters?

(i) The ammeter reading is A

(ii) The voltmeter reading is V

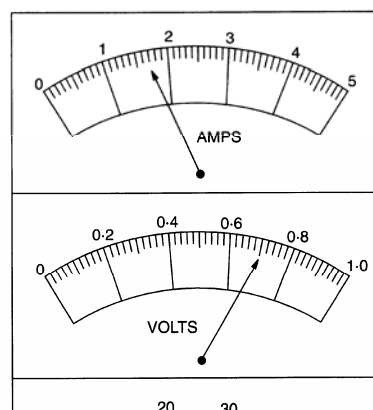


(iii) The milliammeter reading is mA

8 Complete the table

Electrical Quantity		Unit	
Name	Symbol	Name	Symbol
(a)	I	ampere	
(b)	voltage		V
(c)	R		Ω

Section C


1 Look at the circuit diagram below.

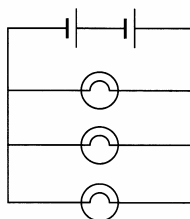


- (a) Show, on the diagram, using symbols, how you would connect,
 (i) an ammeter to measure the total current through the cells,
 (ii) a voltmeter to measure the voltage across one of the 3 bulbs.
 (b) State the type of connection with reference to
 (i) the cells, (ii) bulbs

5 Basic ideas of electricity

2 Study the following circuit diagram.

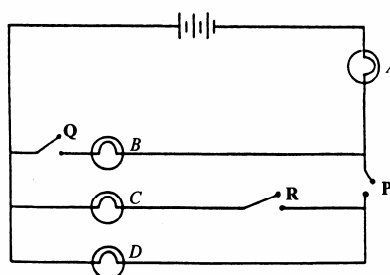

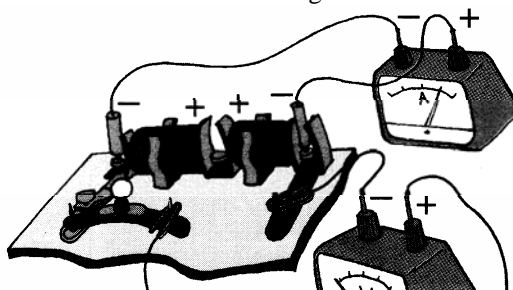- (a) From the above diagram, state which bulbs will light up when
 (i) switches Q and P are closed,
 (ii) switches R and P are closed,
 (iii) only P is closed
 (b) If the three lamps in the above circuit are identical, state the brightness on the three bulbs when all are lit.
- 3 A student set up the circuit shown in the diagram. She wanted to measure: (i) the current through the bulb, and (ii) the voltage across the cells. But the circuit is wrong.



- (a) List the four mistakes.
(b) Draw the correct circuit diagram.
- 4 Draw a circuit diagram to show how two dry cells, a switch and a bulb are connected in series. In the diagram include an ammeter to measure the current and a voltmeter to measure the voltage across the bulb.
- 5 Draw a circuit diagram to represent the electrical circuit as shown.

