


HW.1 - Ch.10

P.13 $d=0.2\text{mm}$, $A=0.08\text{m}^2$, $V=200\text{V}$

- a) $E=V/d=200/0.2\text{mm}=1 \cdot 10^6 \text{ V/m}$
 b) $Q=\epsilon AE=\epsilon_0 \epsilon_r AE=8.85 \cdot 10^{-12} \cdot 7 \cdot 0.08 \cdot 10^6 = 4.956 \mu\text{C}$
 c) $C=\epsilon_r C_0=7 \cdot (\epsilon_0 A/d)=0.0248 \mu\text{F}$, or $C=Q/V=0.024 \mu\text{F}$


P.19

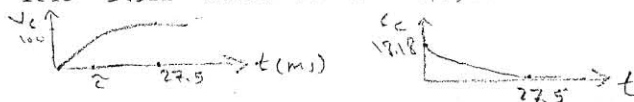- a) $\tau=RC=(R_1+R_2)C=(2.2\text{K}+3.3\text{K}) \cdot 1 \mu\text{F}=5.5\text{ms}$
 b) $V_c=E(1-\exp(-t/\tau))=100(1-\exp(-t/5.5\text{ms}))$
 c) At $t=1\tau$, $V_c=100(1-\exp(-1))=63.21\text{V}$.
 At $t=3\tau$, $V_c=100(1-\exp(-3))=95.02\text{V}$.
 At $t=5\tau$, $V_c=100(1-\exp(-5))=99.33\text{V}$.
 d) $i_c=E/R \exp(-t/\tau)=100/5.5\text{K} \exp(-t/5.5\text{ms})=18.18 \cdot 10^{-3} \exp(-t/5.5\text{ms})$
 $V_R=V_{(R=3.3\text{K})}=RI=R i_c=3.3\text{K} \cdot 18.18 \cdot 10^{-3} = 60\text{V}$, so $V_R=60 \exp(-t/5.5\text{ms})$
 e) sketch of V_c & i_c



P.21

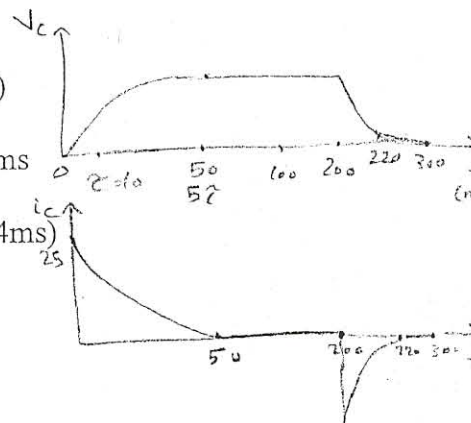- a) $\tau=RC=(3\text{K}+2\text{K}) \cdot 2 \mu\text{F}=10 \text{ ms}$
 b) $V_c=E(1-\exp(-t/\tau))=50(1-\exp(-t/10\text{ms}))$
 c) $i_c=E/R \exp(-t/\tau)=50/5\text{K} \exp(-t/10\text{ms})=10 \cdot 10^{-3} \exp(-t/10\text{ms})$
 d) at $t=100\text{ms}$; $5\tau=5 \cdot 10\text{ms}=50\text{ms}$; ; ; so $V_c=50\text{V}$ & $i_c=0$
 e) at $t=200\text{ms}$ (discharge) , $\tau=R_2 C=2\text{k} \cdot 2\mu\text{F}=4\text{ms}$, $5\tau=20\text{ms}$
 $V_c=E \exp(-t/\tau)=50 \exp(-t/4\text{ms})$
 $i_c=-E/R_2 \exp(-t/\tau)=-50/2\text{K} \exp(-t/4\text{ms})=-25 \cdot 10^{-3} \exp(-t/4\text{ms})$
 f) sketch of V_c & i_c



P.25 $C=1000 \mu\text{F}$, $V=6\text{V}$, $R=0.002\Omega$

- a) $t(\text{discharge})=5\tau=5RC=5(0.002 \cdot 1000 \mu\text{F})=10 \mu\text{sec}$.
 b) $i_c(\text{peak})=E/R=V/R=6/0.002=3000\text{A}$
 c) yes

P.29 $t=?$ when $i_c=1/2 i_{\text{peak}}=1/2 \cdot I_m=1/2 \cdot 3000=1500 \text{ A}$
 $i_c=E/R \exp(-t/RC) \rightarrow 1500=3000 \exp(-t/2 \mu\text{sec}) \rightarrow t=-1.386 \mu\text{sec}$

P.31

$\tau=RC=200 \mu\text{F} \cdot R$, $t=\tau \ln(E/(E-V_c)) \rightarrow \tau=10.91\text{sec}$
 $R=\tau/C=10.91/200 \mu\text{F}=54.567 \text{ K}\Omega$

P.33 $\tau=RC=1 \text{ M} \cdot 0.2 \mu\text{F}=0.2 \text{ sec}$.

- a) $V_c=E(1-\exp(-t/\tau))$
 At $t=0.5\text{s}$, $V_c=60(1-\exp(-.5/.2))=55.075\text{V}$.
 At $t=1\text{s}$, $V_c=60(1-\exp(-1/.2))=59.59\text{V}$.
 $i_c=E/R \exp(-t/\tau)=60/1\text{M} \exp(-t/0.2\text{s})$
 At $t=0.5\text{s}$, $i_c=60/1\text{M} \cdot (\exp(-.5/.2))=4.92 \mu\text{A}$
 At $t=1\text{s}$, $i_c=60/1\text{M} \cdot (\exp(-1/.2))=0.4038 \mu\text{A}$
 $V_{R1}=E \exp(-t/\tau)$
 At $t=0.5\text{s}$, $V_{R1}=60 \cdot (\exp(-.5/.2))=4.92 \text{ V}$
 At $t=1\text{s}$, $V_{R2}=60/1\text{M} \cdot (\exp(-1/.2))=0.4038 \text{ V}$

P.23 $\tau = L/R_{Th} = 10\text{mH}/1.5\text{K} = 6.67\mu\text{s}$

a) $R_{Th} = R_1 \parallel R_2 = 1.498 = 1.5\text{k}\Omega$ & $E_{Th} = V_{R2} = E \cdot R_2 / (R_1 + R_2) = 5.45\text{V}$

$i_L = E_{Th}/R_{Th} (1 - \exp(-t/\tau)) = 3.63 \cdot 10^{-3} (1 - \exp(-t/6.67\mu\text{s}))$

$V_L = E_{Th}(\exp(-t/\tau)) = 5.45(\exp(-t/6.67\mu\text{s}))$

b) at $t = 10\mu\text{s}$, $i_L = 2.82\text{mA}$, $V_L = 1.21\text{V}$

c) $i_L = I_i (\exp(-t/\tau')$ since $\tau' = L/R_2 = 10/4.7\text{k} = 2.128\mu\text{s}$

$i_L = 0.8 \cdot 10^{-3} (\exp(-t/2.128\mu\text{s}))$

$V_L = V_i (\exp(-t/\tau')$ since $V_i = I_i R_2 = 2.128\mu\text{s} \cdot 4.7\text{k} = 13.25\text{V}$

$V_L = -13.25(\exp(-t/2.128\mu\text{s}))$ (($5\tau = 33.35$))

d) sketch of i_L & V_L

P.33 R: $5.7\text{K}\Omega$ & $9.1\text{K}\Omega$, , , , L: 4H & 2H as in the circuit shown.

P.37

$R_T = 25\Omega$

$I_1 = I_T = E/R_T = 50/25 = 2\text{A}$

$I_2 = 6 I_T / (6+3) = 12/9 = 1.33\text{A}$

$V_1 = 10\text{V}$. by KVL or $(3+2) \cdot 2 = 10\text{V}$

P.40

$W_{L1} = \frac{1}{2} L_1 \cdot I_{L1}^2 = \frac{1}{2} \cdot 0.5 \cdot (2)^2 = 1\text{J}$

$W_{L2} = \frac{1}{2} L_2 \cdot I_{L2}^2 = \frac{1}{2} \cdot 4 \cdot (1.33)^2 = 3.54\text{J}$

P.23 $\tau = L/R_{Th} = 10\text{mH}/1.5\text{K} = 6.67\mu\text{s}$

a) $R_{Th} = R_1 \parallel R_2 = 1.498 = 1.5\text{k}\Omega$ & $E_{Th} = V_{R2} = E \cdot R_2 / (R_1 + R_2) = 5.45\text{V}$

$i_L = E_{Th}/R_{Th} (1 - \exp(-t/\tau)) = 3.63 \cdot 10^{-3} (1 - \exp(-t/6.67\mu\text{s}))$

$V_L = E_{Th}(\exp(-t/\tau)) = 5.45(\exp(-t/6.67\mu\text{s}))$

b) at $t = 10\mu\text{s}$, $i_L = 2.82\text{mA}$, $V_L = 1.21\text{V}$

c) $i_L = I_i (\exp(-t/\tau')$ since $\tau' = L/R_2 = 10/4.7\text{k} = 2.128\mu\text{s}$

$i_L = 0.8 \cdot 10^{-3} (\exp(-t/2.128\mu\text{s}))$

$V_L = V_i (\exp(-t/\tau')$ since $V_i = I_i R_2 = 2.128\mu\text{s} \cdot 4.7\text{k} = 13.25\text{V}$

$V_L = -13.25(\exp(-t/2.128\mu\text{s}))$ (($5\tau = 33.35$))

d) sketch of i_L & V_L

P.33 R: $5.7\text{K}\Omega$ & $9.1\text{K}\Omega$, , , , L: 4H & 2H as in the circuit shown.

P.37

$R_T = 25\Omega$

$I_1 = I_T = E/R_T = 50/25 = 2\text{A}$

$I_2 = 6 I_T / (6+3) = 12/9 = 1.33\text{A}$

$V_1 = 10\text{V}$. by KVL or $(3+2) \cdot 2 = 10\text{V}$

P.40

$W_{L1} = \frac{1}{2} L_1 \cdot I_{L1}^2 = \frac{1}{2} \cdot 0.5 \cdot (2)^2 = 1\text{J}$

$W_{L2} = \frac{1}{2} L_2 \cdot I_{L2}^2 = \frac{1}{2} \cdot 4 \cdot (1.33)^2 = 3.54\text{J}$

HW.2 – Ch.12

P.9 $V = L di/dt$, $L=200\text{mH} = 0.2\text{H}$

$t = 0 > 3 \text{ ms}$,,, $V = 0$
$t = 3 > 8 \text{ ms}$,,, $V = 0.2 * 40\text{m}/5\text{m} = 1.6\text{V}$
$t = 8 > 13 \text{ ms}$,,, $V = 0.2 * -40\text{m}/5\text{m} = -1.6\text{V}$
$t = 13 > 14 \text{ ms}$,,, $V = 0$
$t = 14 > 15 \text{ ms}$,,, $V = 0.2 * 40\text{m}/1\text{m} = 8\text{V}$
$t = 15 > 16 \text{ ms}$,,, $V = 0.2 * -40\text{m}/1\text{m} = -8\text{V}$
$t = 16 > 0$,,, $V = 0$

((sketch of VL))

P.13

a) $\tau = L/R = 5\text{mH}/2.2\text{K} = 2.27\mu\text{s}$
 b) $i_L = E/R(1 - \exp(-t/\tau)) = 12/2.2\text{k}(1 - \exp(-t/2.27\mu\text{s})) = 5.45 * 10^{-3}(1 - \exp(-t/2.27\mu\text{s}))$
 c) $V_L = E(\exp(-t/\tau)) = 12(\exp(-t/2.27\mu\text{s}))$
 $V_R = E(1 - \exp(-t/\tau)) = 12(1 - \exp(-t/2.27\mu\text{s}))$
 d) At $t = 1\tau$,, $i_L = 3.45\text{mA}$, $V_L = 4.414\text{V}$.
 At $t = 3\tau$,, $i_L = 5.179\text{mA}$, $V_L = 0.597\text{V}$.
 At $t = 5\tau$,, $i_L = 5.413\text{mA}$, $V_L = 0.081\text{V}$. ($5\tau = 11.35\mu\text{sec}$)
 e) sketch of i_L , V_L & V_R

P.15 $\tau = L/R_1 = 5\text{mH}/6.8\text{K} = 0.735\mu\text{s}$

a) $i_L = E/R_1 (1 - \exp(-t/\tau)) = 0.882 * 10^{-3}(1 - \exp(-t/0.735\mu\text{s}))$
 $V_L = E(\exp(-t/\tau)) = 6(\exp(-t/0.735\mu\text{s}))$
 b) $i_L = I_m (\exp(-t/\tau')$ since $I_m = E/R_1 = 6/6.8\text{k} = 0.882\text{mA}$ & $\tau' = L/(R_1 + R_2) = 0.33 \mu\text{s}$
 $i_L = 0.882 * 10^{-3}(\exp(-t/0.33\mu\text{s}))$
 $V_L = V_i (\exp(-t/\tau')$ since $V_i = (1 + R_2/R_1) E = 13.23\text{V}$
 $V_L = -13.23 (\exp(-t/0.33\mu\text{s}))$ (($5\tau = 3.675$ & $5\tau' = 1.65$))
 c) sketch of i_L & V_L

d) $V_{R2} = -R_2/R_1 E (\exp(-t/\tau'))$
 $= -7.235 \exp(-t/0.33\mu\text{s})$

sketch of V_{R2}

- b) $10\text{min} = 10 \cdot 60 = 600\text{s}$, $5\tau = 5 \cdot 0.2 = 1\text{s}$, i.e. full charged, $\tau_{\text{discharge}} = (R_1 + R_2)C = 5\text{M}\Omega \times 0.2\mu\text{F} = 1\text{s}$.
 Find t when $i_c = 8\mu\text{A}$, $t = \tau \ln(E/i_c R) = 1 \ln(60/(8\mu \cdot 5\text{M})) = 0.405\text{sec}$.
 Find t when $V_c = 10\text{V}$, $t = \tau \ln(E/V_c) = 1 \ln(60/10) = 1.795\text{sec}$.

P.35

- a) $V_c = ?$ At $t = 4\tau$ find R_{Th} & E_{Th}

$$R_{\text{Th}} = R + R_{\text{in}} = 12\text{M} \quad \text{,,} \quad E_{\text{Th}} = 10\text{M} \cdot 24 / (10\text{M} + 2\text{M}) = 20\text{V}$$

$$\tau = R_{\text{Th}} C = 12\text{M} \cdot 1\mu\text{F} = 12\text{s}$$

$$V_c = ? \quad \text{at } t = 4\tau = 48\text{s}$$


$$V_c = E_{\text{Th}} (1 - \exp(-t/\tau)) = 20(1 - \exp(-4)) = 19.633\text{V}$$

- b) $t = ?$,, $i_c = 3\mu\text{A}$

$$t = \tau \ln(E_{\text{Th}} / i_c R_{\text{Th}}) = 12 \ln(20 / (3\mu \cdot 12\text{M})) = 7.053\text{sec} \quad (\text{not same as book answer})$$

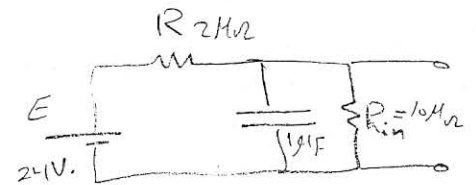- c) $t = ?$,, $V_c = 10\text{V}$

$$t = \tau \ln(E_{\text{Th}} / (E_{\text{Th}} - V_c)) = 12 \ln(20 / (20 - 10)) = 8.3177\text{sec} \quad (\text{not same as book answer})$$



P.41 $i_{c\text{av}} = C \Delta V / \Delta t$

$$t = 0 \rightarrow 4\text{ms} \quad \text{,,} \quad i_c = 0.06\mu [20/4\text{m}] = 0.3\text{mA}$$

$$t = 4 \rightarrow 6\text{ms} \quad \text{,,} \quad i_c = 0.06\mu [(50-20)/2\text{m}] = 0.9\text{mA}$$


$$t = 6 \rightarrow 7\text{ms} \quad \text{,,} \quad i_c = 0.06\mu [(100-50)/1\text{m}] = 3\text{mA}$$

$$t = 7 \rightarrow 10\text{ms} \quad \text{,,} \quad i_c = 0$$

$$t = 10 \rightarrow 13\text{ms} \quad \text{,,} \quad i_c = 0.06\mu [(-50-100)/3\text{m}] = -3.2\text{mA}$$

$$t = 13 \rightarrow 15\text{ms} \quad \text{,,} \quad i_c = 0.06\mu [0 - (-60)/2\text{m}] = 1.8\text{mA}$$
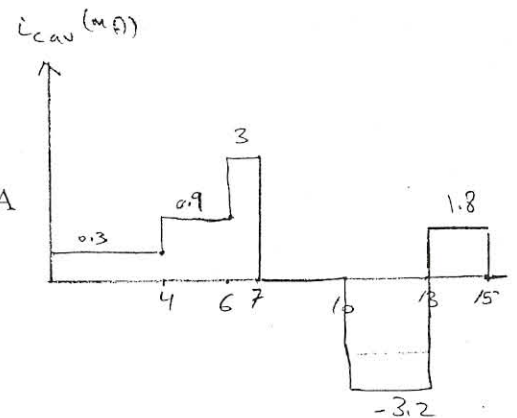
$$t > 15\text{ms} \quad \text{,,} \quad i_c = 0$$



P.45(a)

$$C_{23} = C_2 C_3 / C_2 + C_3 = 4\mu\text{F} \quad \text{,,} \quad C_T = C_1 + C_{23} = 6 + 4 = 10\mu\text{F}$$

$$E = V_{23} = V_1 = 10\text{V}$$

$$Q_1 = V_1 C_1 = 10 \cdot 6\mu = 60\mu\text{C}$$


$$V_{23} = V_2 + V_3 = 10\text{V}$$

$$Q_{23} = V_{23} C_{23} = 10 \cdot 4 = 40\mu\text{C}$$

$$Q_{23} = Q_2 = Q_3 = 40\mu\text{C}$$

$$V_2 = Q_2 / C_2 = 40\mu / 6\mu = 6.67\text{V}$$
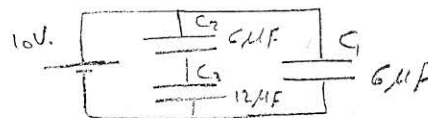
$$V_3 = Q_3 / C_3 = 40\mu / 12\mu = 3.33\text{V}$$



P.51 $C = 1000\mu\text{F}$, $V = 100\text{V}$

a) $W_c = \frac{1}{2} C V^2 = 5\text{J}$

b) $Q = C V = 0.1\text{C}$

c) $t = 1/2000\text{s}$, $i_{c\text{av}} = C \Delta V / \Delta t = 1000\mu \cdot 100 / (1/2000) = 200\text{A}$

d) $P = W_c / t = 5 / (1/2000) = 10,000\text{W} = 10\text{KW}$

e) $i_{\text{max}} = 10\text{mA}$

$$i_{\text{max}} = C \Delta V / \Delta t$$

$$10\text{mA} = 1000\mu \cdot 100 / \Delta t$$

$$\Delta t = 10\text{sec}$$