

# Solution

## Midterm (2)


Name: \_\_\_\_\_

Date: \_\_\_\_\_

### Problem-1:

For this Series-parallel circuit, find the current and voltage at each resistor.

25


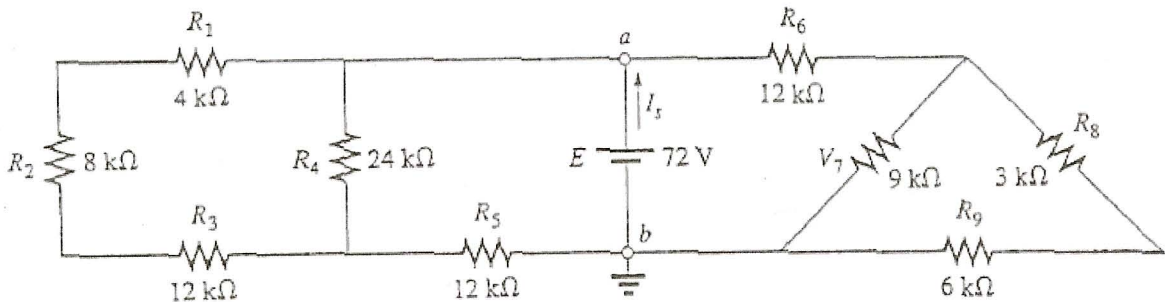


### Solution-1:

①  $R_T = 24k\Omega \parallel 16.5k\Omega$

$$R_T = \frac{24k\Omega \times 16.5k\Omega}{24k\Omega + 16.5k\Omega} = 9.78k\Omega$$

$R_T = 9.78k\Omega$

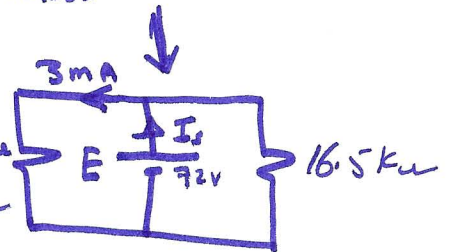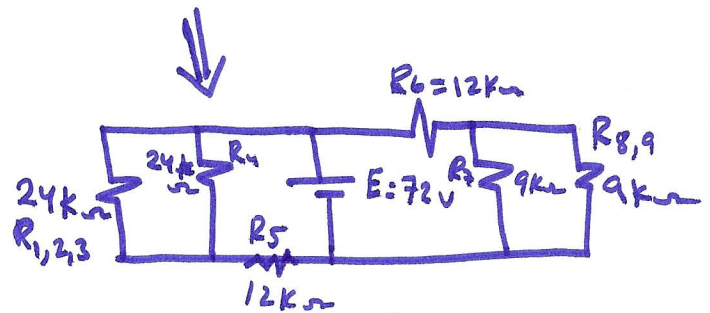

②  $I_5 = \frac{E}{R_T} = \frac{72V}{9.78k\Omega} = 7.36mA \Rightarrow I_5 = 7.36mA$

③  $I_5 = \frac{E}{24k\Omega} = \frac{72V}{24k\Omega} = 3 \times 10^{-3}A = 3mA \Rightarrow I_5 = 3mA$

④  $I_6 = \frac{E}{16.5k\Omega} = \frac{72V}{16.5k\Omega} = 4.36 \times 10^{-3}A = 4.36mA \Rightarrow I_6 = 4.36mA$

⑤  $I_{1,2,3} = \frac{3A}{2} = 1.5A \Rightarrow I_4 = 1.5mA$

⑥  $I_7 = \frac{4.36mA}{2} = 2.18mA \Rightarrow I_8 = I_9 = 2.18mA$

⑦  $V_1 = R_1 \times I_1 = 4k\Omega \times 1.5mA = 6V \Rightarrow V_1 = 6V$

$V_2 = 8k\Omega \times 1.5mA = 12V \Rightarrow V_2 = 12V$

$V_3 = 12k\Omega \times 1.5mA = 18V \Rightarrow V_3 = 18V$

$V_4 = 24k\Omega \times 1.5mA = 36V \Rightarrow V_4 = 36V$

$V_5 = 12k\Omega \times 3mA \Rightarrow V_5 = 36V$

$V_6 = 12k\Omega \times 4.36mA \Rightarrow V_6 = 52.32V$

$V_7 = 9k\Omega \times 2.18mA \Rightarrow V_7 = 19.62V$

$V_8 = 3k\Omega \times 2.18mA = 6.54V$

$V_9 = 6k\Omega \times 2.18mA = 13.08V$

Midterm (2)


Name: \_\_\_\_\_

Date: \_\_\_\_\_

**Problem-2:**


For the circuit shown, find the following:

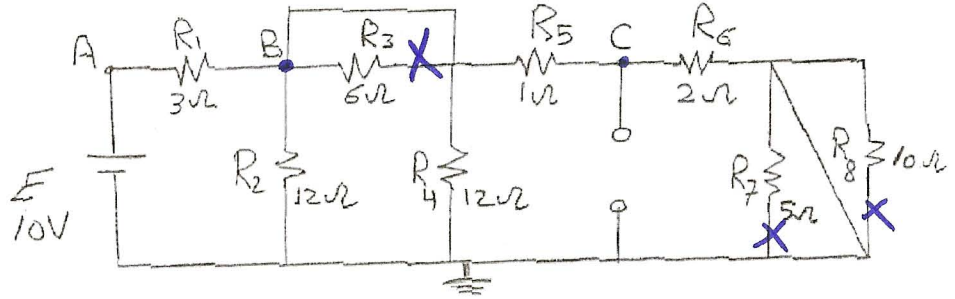1.  $R_T$ .
2.  $I_1$ .
3.  $I_4$  by using (CDR).
4.  $V_2$  by using (VDR).
5.  $V_{BC}$ .
6.  $P_5$ .
7.  $P_{del}$ .
8.  $V_{CA}$ .



**Solution-2:**



①  $R_T = 5\Omega$

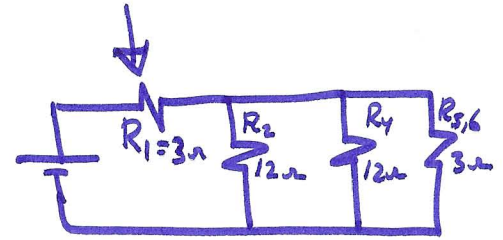

②  $I_1 = \frac{E}{R_T} = \frac{10V}{5\Omega} = 2A \Rightarrow I_1 = 2A$

③  $I_4 = \frac{R_T''}{R_4} I_1 = \frac{2 \times 2}{12} = \frac{4}{12} = \frac{1}{3} \Rightarrow I_4 = \frac{1}{3}A$

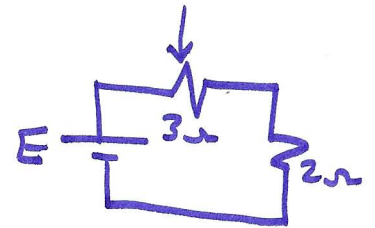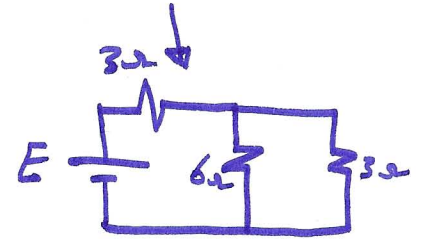OR  $I_{2,4} = \frac{3 \times 2}{6+3} = \frac{6}{9} = \frac{2}{3}A \Rightarrow \begin{cases} I_2 = \frac{1}{3}A \\ I_4 = \frac{1}{3}A \end{cases}$



④  $V_2 = R_T'' \cdot E = \frac{2 \times 10V}{5\Omega} = 4V \Rightarrow V_2 = 4V$

⑤  $V_{BC} = V_B - V_C = V_{R5} = I_5 \times R_5 = \frac{4}{3} \times 1\Omega = 1.33V$

OR  $V_{BC} = R_4 \cdot I_4 - R_6 \cdot I_6$   
 $V_{BC} = (12\Omega) \times (\frac{1}{3}A) - (2\Omega) \times (\frac{4}{3}A) = 4 - \frac{8}{3} = 1.33V \Rightarrow V_{BC} = 1.33V$

⑥  $P_5 = R_5 \times I_5^2 = 1 \times (\frac{4}{3})^2 = \frac{16}{9} = 1.78W \Rightarrow P_5 = 1.78W$

⑦  $P_{del} = I_1 E = 2A \times 10V = 20Watt \Rightarrow P_{del} = 20Watt$

⑧  $V_{CA} = V_C - V_A \Rightarrow V_{CA} = \frac{8}{3}V - 10V \Rightarrow V_{CA} = 2.67V - 10V = -7.33V \Rightarrow V_{CA} = -7.34V$

Midterm (2)


Name: \_\_\_\_\_

Date: \_\_\_\_\_

Problem-3:

For the circuit shown, calculate the following:

1.  $R_T$ .
2.  $I_T$ .

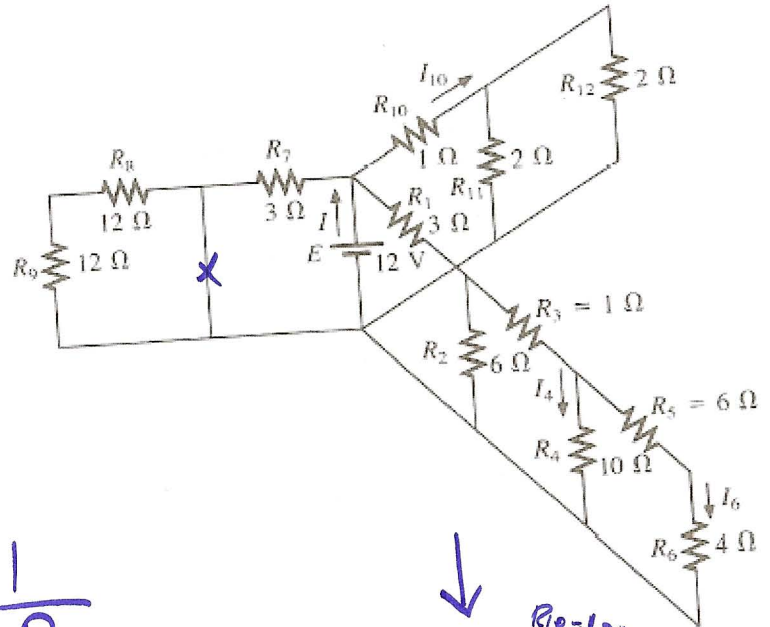

Solution-3:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_T} = \frac{1}{3\Omega} + \frac{1}{2\Omega} + \frac{1}{6\Omega}$$

$$\frac{1}{R_T} = \frac{2+3+1}{6} = \frac{6}{6} = 1$$

$R_T = 1\Omega$

$$I_t = \frac{E}{R_T} = \frac{12V}{1\Omega} = 12A$$

$I_t = 12A$

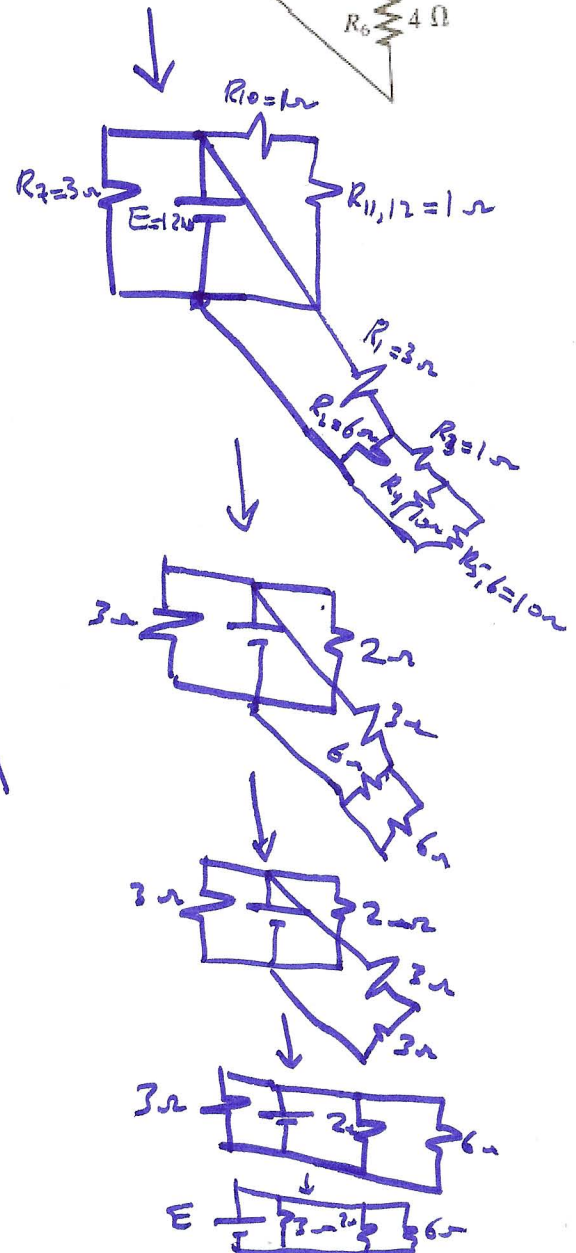

Midterm (2)


Name: \_\_\_\_\_

Date: \_\_\_\_\_

Problem-4:

For the circuit shown, calculate the following:

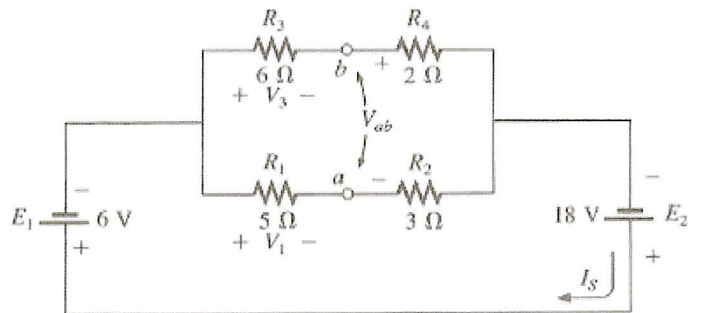
1.  $V_1$ .
2.  $V_3$ .
3.  $V_{ab}$ .
4.  $I_s$ .



Solution-4:

$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(5\Omega) \times (12V)}{(5\Omega) + (3\Omega)} = \frac{60V}{8}$$

$$V_1 = 7.5V$$

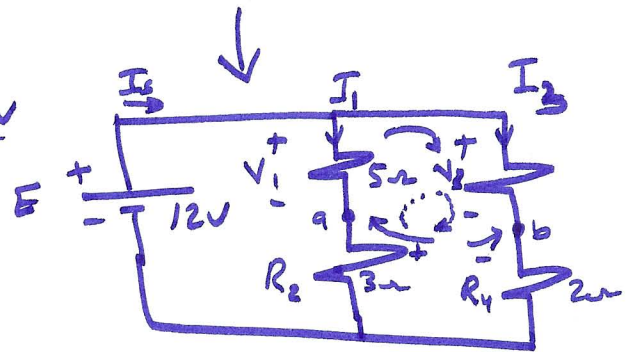

$$V_3 = \frac{R_3 E}{R_3 + R_4} = \frac{(6\Omega) \times (12V)}{(6\Omega) + (2\Omega)} = \frac{72V}{8} = 9V$$

$$V_3 = 9V$$

From the simple figure, with clockwise direction starting at terminal (a)

$$+V_1 - V_3 + V_{ab} = 0 \quad \text{--- (KVL)}$$

$$V_{ab} = V_3 - V_1$$

$$V_{ab} = 9V - 7.5V = 1.5V \Rightarrow V_{ab} = 1.5V$$

By Ohm's Law:

$$I_1 = \frac{V_1}{R_1} = \frac{7.5V}{5\Omega} = 1.5A \Rightarrow I_1 = 1.5A$$

$$I_3 = \frac{V_3}{R_3} = \frac{9V}{6\Omega} = 1.5A \Rightarrow I_3 = 1.5A$$

By (KCL)

$$I_s = I_1 + I_3 \Rightarrow I_s = 1.5A + 1.5A = 3A$$

$$I_s = 3A$$

# Solution


College of Technological Studied, Electronics Department

Electrical Circuits (ENT#140)

Quiz (6)

Name: \_\_\_\_\_


Date: \_\_\_\_\_

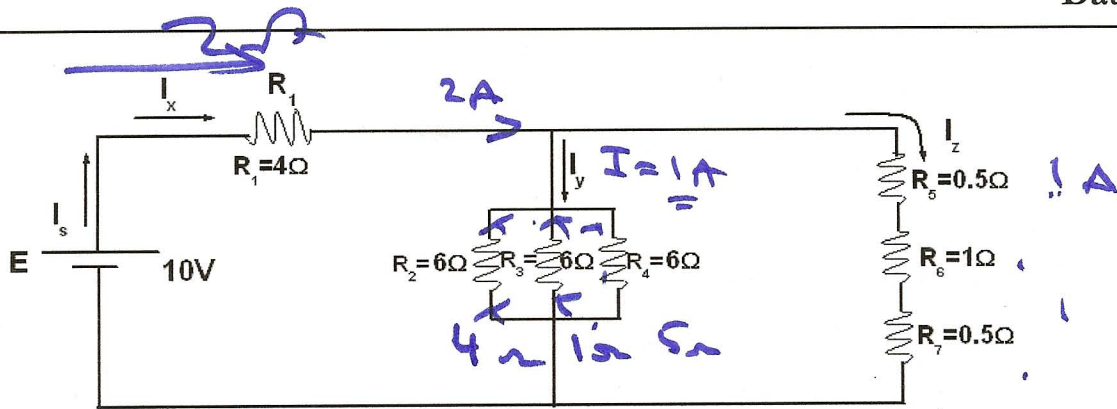

Q) For the circuit shown, calculate:

- a.  $R_T$ .
- b.  $I_s$ .
- c.  $I_x$ .
- d.  $I_y$ .
- e.  $I_z$ .
- ~~f.  $V_{R1}$ .~~
- g.  $V_{R1}$ .
- h.  $V_{R3}$ .
- i.  $V_{R7}$ .

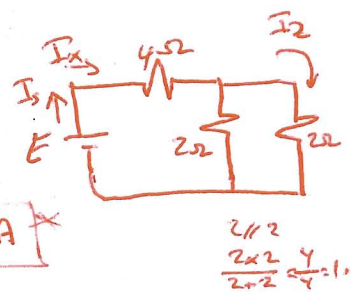a)  $R_T = 4 + 1 = 5\Omega$   
 $R_T = 5\Omega$



b)  $I_s = \frac{E}{R_T} = \frac{10V}{5\Omega} = 2A$

c)  $I_x = I_s = 2A$

d)  $I_y = \frac{2}{2} = 1A \Rightarrow$  OR  $I_y = \frac{R_T \cdot I_s}{R_{1,3,4}}$

e)  $I_z = \frac{2}{2} = 1A$   $I_y = \frac{1 \times 2}{2} = 1A$

f)  $V_{R1} = R_1 I_x = 4\Omega \times 2A = 8V$  OR  $V_{R1} = \frac{R_1 E}{R_T}$

$V_{R1} = \frac{4 \times 10}{5} = \frac{40}{5} = 8V$

g)  $V_{R3} = 2\Omega \times 1A = 2V$

$V_{R3} = R_3 \times I_{R3}$   
 $= 6\Omega \times \frac{1}{3}A = 2V$

h)  $V_{R7} = 0.5\Omega \times I_z$

$5 \cdot 0.5\Omega \times 1A$   
 $V_{R7} = 0.5V$

$4\Omega \times \frac{1}{3} =$