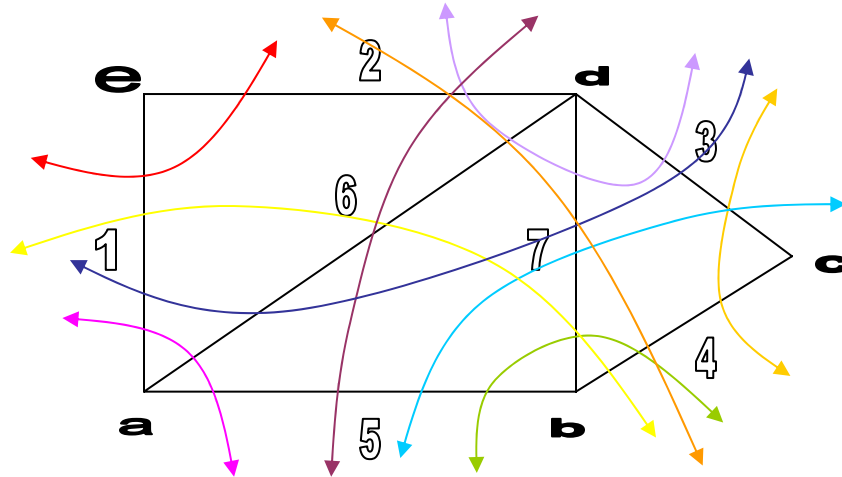


THIS SOLUTION WILL BE MADE AVAILABLE ONLINE
AT http://www.geocities.com/ezy447/assign1-06_ans.pdf
AFTER 5PM, FRIDAY, SEPTEMBER 8, 2006

- Date of submission: on or before 5.00pm, 12th September 2006.
- You should submit your assignment to your respective tutor.
- Each question carries **15 marks**. You should attend all the questions

Question 1


- a) List **ten** cut-sets of the following graph:



- b) Derive the equations of the following network in terms of:

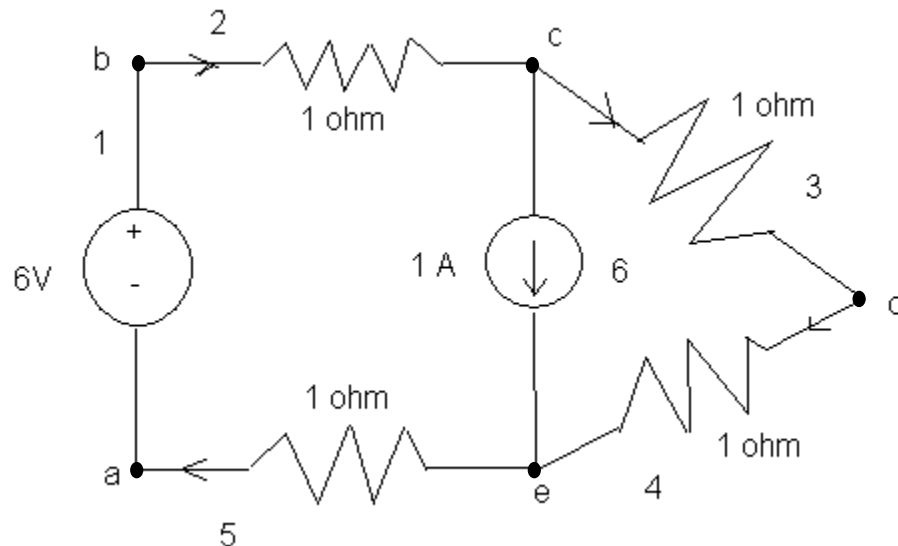
- (i) Chord currents.
- (ii) Branch voltages;

(Hint: take the tree as { 1 , 2 , 3 , 4 }).



Assignment
ECT2036: CIRCUITS AND SIGNALS

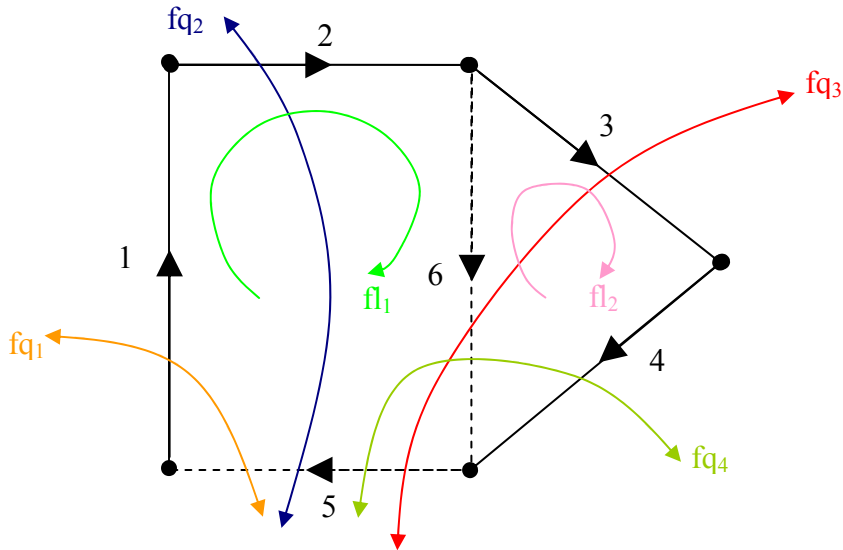If we take tree branches as 1, 2, 3, 4 then co-tree branches are 5 and 6. The graph of this tree becomes:



Fundamental cut-sets:

Fundamental cut-set 1: $f_{q1}: \{1, 5\}$

Fundamental cut-set 2: $f_{q2}: \{2, 5\}$

Fundamental cut-set 3: $f_{q3}: \{3, 6, 5\}$

Fundamental cut-set 4: $f_{q4}: \{4, 6, 5\}$

From fundamental cut-sets we obtained, we can derive the chord current equations. We define current entering the node as positive and current leaving the node as negative.

From f_{q1} : $i_5 - i_1 = 0$

From f_{q2} : $i_2 - i_5 = 0$

From f_{q3} : $i_3 + i_6 - i_5 = 0$

From f_{q4} : $i_4 + i_6 - i_5 = 0$

Fundamental loops:

Fundamental loop 1: $f_{l1}: \{5, 1, 2, 3, 4\}$

Fundamental loop 2: $f_{l2}: \{6, 3, 4\}$

For fundamental loop voltage equations, we treat branch orientated in the same loop direction as positive and branch opposed the loop direction as negative.

From f_{l1} : $v_5 + v_1 + v_2 + v_3 + v_4 = 0$


From f_{l2} : $-v_6 + v_3 + v_4 = 0$

Assignment
ECT2036: CIRCUITS AND SIGNALS

Question 2

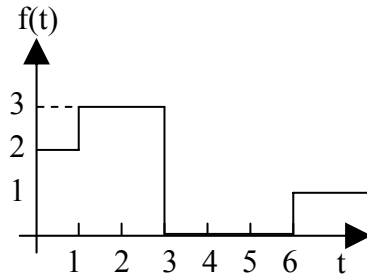a) Sketch the waveform

$$f(t) = 2u(t) + u(t-1) - 3u(t-2) + u(t-3).$$



b) Determine whether $f(t) = e^{-t} [u(t) + u(t-1)]$ is an energy signal ?

Please do this part
on your own as
you should get an
Energy signal

$$\begin{aligned} \text{Energy, } E &= \int_{-\infty}^{\infty} f^2(t) dt = \int_{-\infty}^{\infty} (e^{-t})^2 [u(t) + u(t-1)]^2 dt \\ &= \int_{-\infty}^{\infty} e^{-2t} 2^2 dt = 4 \int_{-\infty}^{\infty} e^{-2t} dt = 2e^{-2t} \Big|_{-\infty}^{\infty} = 2(0) - 2(\infty) = -\infty \end{aligned}$$

$f(t) = e^{-t} [u(t) + u(t-1)]$ is ~~NOT~~ an energy signal

c) Are the functions given in (a) & (b) even or odd ?

For $f(t) = 2u(t) + u(t-1) - 3u(t-2) + u(t-3)$

$$\begin{aligned} \text{To test for even: } f(-t) &= 2u(-t) + u(-t-1) - 3u(-t-2) + u(-t-3) \\ &= -2u(t) - u(t+1) + 3u(t+2) - u(t+3) \\ &= \text{not an even function} \end{aligned}$$

$$\begin{aligned} \text{To test for odd: } -f(-t) &= -\{2u(-t) + u(-t-1) - 3u(-t-2) + u(-t-3)\} \\ &= -\{-2u(t) - u(t+1) + 3u(t+2) - u(t+3)\} \\ &= 2u(t) + u(t-1) - 3u(t-2) + u(t-3) \\ &= f(t) \\ &= \text{an odd function} \end{aligned}$$

For $f(t) = e^{-t} [u(t) + u(t-1)]$

$$\begin{aligned} \text{To test for even: } f(-t) &= e^t [u(-t) + u(-t-1)] \\ &= e^t [-u(t) - u(t+1)] \\ &= -u(t)e^t - u(t+1)e^t \\ &= -e^t [u(t) + u(t+1)] \\ &= \text{not an even function} \end{aligned}$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

To test for odd: $-f(-t) = -\{e^t[u(-t)+u(-t-1)]\}$
 $= -\{e^t[-u(t)-u(t+1)]\}$
 $= -\{-u(t)e^t - u(t+1)e^t\}$
 $= -\{-e^t[u(t)+u(t+1)]\}$
 $= e^t[u(t)+u(t+1)]$
 $= \text{not an odd function}$

d) Carry out discrete time convolution at, $n = 5$ for

$$f_1[n] = (-1)^n \{u[n] + u[n-1]\};$$

$$f_2[n] = n \{ \delta[n] + 2u[n-1] - u[n-2] \}$$

For discrete-time convolution,

$$c[n] = \sum_{k=0}^n f_1[k]f_2[n-k] \Rightarrow c[n] = \sum_{k=0}^n f_1[k]f_2[n-k]$$

$$c[5] = \sum_{k=0}^5 f_1[k]f_2[5-k]$$

$$= f_1[0]f_2[5] + f_1[1]f_2[4] + f_1[2]f_2[3] + f_1[3]f_2[2] + f_1[4]f_2[1] + f_1[5]f_2[0]$$

$$= 1(5) + (-2)(4) + 2(3) + (-2)(2) + 2(2) + (-2)(0)$$

$$= 5 - 8 + 6 - 4 + 4 - 0$$

$$= 3$$

Question 3

a) Determine the Fourier series for the periodic function shown in Figure Q3a.

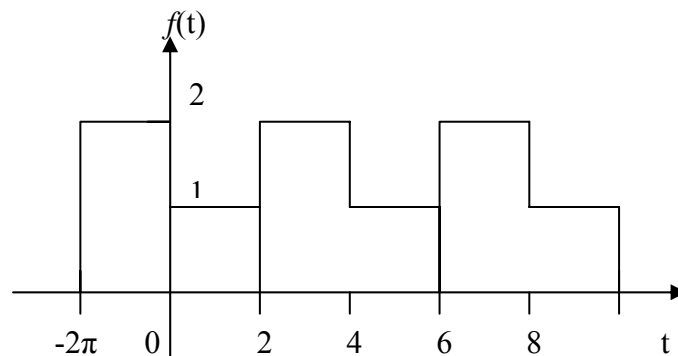


Figure Q3a

Since $T=4$; $\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{4} = \frac{\pi}{2}$, thus

Fourier coefficients:

$$A_0 = \frac{1}{T} \int_0^T f(t)dt = \frac{1}{4} \left[\int_{-2}^0 2dt + \int_0^2 1dt \right] = \frac{1}{4} [2t|_{-2}^0 + t|_0^2] = \frac{1}{4} (4 + 2) = \frac{3}{2}$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

Fourier cosine coefficients:

$$\begin{aligned}
 A_n &= \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt = \frac{2}{4} \left[\int_{-2}^0 2 \cos n \frac{\pi}{2} t dt + \int_0^2 \cos n \frac{\pi}{2} t dt \right] \\
 &= \frac{1}{2} \left[2 \int_{-2}^0 \cos n \frac{\pi}{2} t dt + \int_1^2 \cos n \frac{\pi}{2} t dt \right] \\
 &= \left[\frac{\sin n \frac{\pi}{2} t}{n \frac{\pi}{2}} \right]_{-2}^0 + \frac{1}{2} \left[\frac{\sin n \frac{\pi}{2} t}{n \frac{\pi}{2}} \right]_1^2 \\
 &= 0
 \end{aligned}$$

Fourier sine coefficients:

$$\begin{aligned}
 B_n &= \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt = \frac{2}{4} \left[\int_{-2}^0 2 \sin n \frac{\pi}{2} t dt + \int_0^2 \sin n \frac{\pi}{2} t dt \right] \\
 &= \frac{1}{2} \left[2 \int_{-2}^0 \sin n \frac{\pi}{2} t dt + \int_1^2 \sin n \frac{\pi}{2} t dt \right] \\
 &= - \left[\frac{\cos n \frac{\pi}{2} t}{n \frac{\pi}{2}} \right]_{-2}^0 - \frac{1}{2} \left[\frac{\cos n \frac{\pi}{2} t}{n \frac{\pi}{2}} \right]_1^2 \\
 &= \frac{(-1)^n - 1}{2n\pi} + \frac{(-1)^n - 1}{n\pi} \\
 &= -\frac{1}{n\pi} \left[\frac{(-1)^n}{2} + (-1)^n \right] \\
 &\quad (\cos n\pi = -1 \text{ if } n \text{ is odd})
 \end{aligned}$$

The Fourier series can be written as:

$$f(t) = A_0 + \sum_{n=1}^{\infty} A_n \cos n\omega_0 t + \sum_{n=1}^{\infty} B_n \sin n\omega_0 t$$

Substituting the Fourier coefficients yields:

$$f(t) = \frac{3}{2} - \sum_{n=1}^{\infty} \frac{1}{n\pi} \left[\frac{(-1)^n}{2} + (-1)^n \right] \sin n \frac{\pi}{2} t$$

b) For the circuit of Figure Q3b, the applied voltage $V(t)$ is given to the circuit as

$$V(t) = 3 + 5.4 \cos(100\pi - 45^\circ) + 3.82 \cos(200\pi - 90^\circ) + 1.8 \cos(300\pi - 135^\circ).$$

Find:

Assignment
ECT2036: CIRCUITS AND SIGNALS

i) The current flowing through the resistors, $I(t)$.

For calculating the current, $I(t)$ flowing in the circuit, we have to calculate the circuit impedances at all the frequencies for which the signal components are present in the applied voltage.

The applied voltage consists of dc component, fundamental, second harmonic and third harmonic components. The fundamental frequency, $\omega = 100\pi$

Impedance at zero frequency (dc):

$$|Z_0| = R = R_1 + R_2 = (15 + 15)\Omega = 30\Omega \quad \text{Phase angle, } \delta_0 = 0^\circ$$

$$I_0 = \frac{V_0}{R} = \frac{3}{30} = 0.1A$$

Impedance at fundamental frequency ($\omega = 100\pi$)

$$Z_1 = R^2 + j\omega L$$

$$|Z_1| = \sqrt{R^2 + \omega^2 L^2} = \sqrt{900 + 986.96} = \sqrt{1886.96} = 43.44\Omega$$

$$\text{Phase angle, } \delta_1 = \tan^{-1} \frac{\omega L}{R} = \tan^{-1} \frac{100\pi \times 0.1}{30} = 46.32^\circ$$

Impedance at second harmonic frequency ($2\omega = 200\pi$)

$$Z_2 = R^2 + j(2\omega L)$$

$$|Z_2| = \sqrt{R^2 + 4\omega^2 L^2} = \sqrt{900 + 3947.842} = \sqrt{4847.842} = 69.63\Omega$$

$$\text{Phase angle, } \delta_2 = \tan^{-1} \frac{2\omega L}{R} = \tan^{-1} \frac{200\pi \times 0.1}{30} = 64.48^\circ$$

Impedance at third harmonic frequency ($3\omega = 300\pi$)

$$Z_3 = R^2 + j(3\omega L)$$

$$|Z_3| = \sqrt{R^2 + 9\omega^2 L^2} = \sqrt{900 + 15791.367} = \sqrt{8882.64} = 94.25\Omega$$

$$\text{Phase angle, } \delta_3 = \tan^{-1} \frac{3\omega L}{R} = \tan^{-1} \frac{300\pi \times 0.1}{30} = 72.34^\circ$$

Thus:

$$I(t) = I_0(t) + I_1(t) + I_2(t) + I_3(t)$$

$$= \frac{V_0}{R} + \frac{V_1}{|Z_1|} \cos(\omega t - \delta_1) + \frac{V_2}{|Z_2|} \cos(\omega t - \delta_2) + \frac{V_3}{|Z_3|} \cos(\omega t - \delta_3)$$

$$I(t) = \frac{3}{30} + \frac{5.4}{43.44} \cos(100\pi t - 91.32^\circ) + \frac{3.82}{69.63} \cos(200\pi t - 154.48^\circ) + \frac{1.8}{94.25} \cos(300\pi t - 207.34^\circ)$$

$$I(t) = 0.1 + 0.124 \cos(100\pi t - 91.32^\circ) + 0.055 \cos(200\pi t - 154.48^\circ) + 0.019 \cos(300\pi t - 207.34^\circ)$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

ii) The I_{rms} and V_{rms}

$$\begin{aligned} I_{rms} &= \sqrt{\frac{V_0^2}{R_0^2} + \frac{1}{2} \frac{V_1^2}{|Z_1|^2} + \frac{1}{2} \frac{V_2^2}{|Z_2|^2} + \frac{1}{2} \frac{V_3^2}{|Z_3|^2}} \\ &= \sqrt{(0.1)^2 + \frac{1}{2}(0.124)^2 + \frac{1}{2}(0.055)^2 + \frac{1}{2}(0.019)^2} \\ &= \sqrt{0.0194} \\ &= 0.139A \end{aligned}$$

$$\begin{aligned} V_{rms} &= \sqrt{V_0^2 + \frac{V_1^2}{2} + \frac{V_2^2}{2} + \frac{V_3^2}{2}} \\ &= \sqrt{3^2 + \frac{5.4^2}{2} + \frac{3.82^2}{2} + \frac{1.8^2}{2}} \\ &= \sqrt{32.496} \\ &= 5.7V \end{aligned}$$

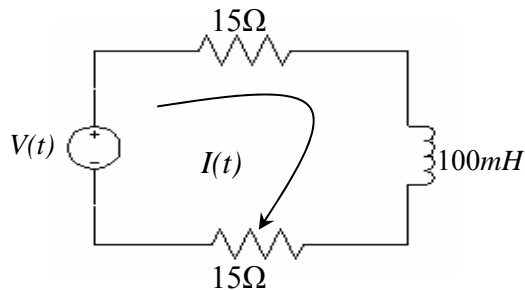


Figure Q3b

Question 4

a) Find the inverse Laplace Transform of the following functions:

(i) $F(s) = \frac{4s + 5}{(s + 1)(s + 2)^2}$

By using partial fraction:

$$\begin{aligned} \frac{4s + 5}{(s + 1)(s + 2)^2} &= \frac{A}{(s + 2)^2} + \frac{B}{(s + 2)} + \frac{C}{(s + 1)} \\ &= \frac{A(s + 1) + B(s + 2)(s + 1) + C(s + 2)^2}{(s + 2)^2(s + 1)} \end{aligned}$$

$$\Rightarrow 4s + 5 = A(s + 1) + B(s + 2)(s + 1) + C(s + 2)^2$$

For $s = -1$: $4(-1) + 5 = C$; $C = 1$

For $s = -2$: $4(-2) + 5 = -A$; $A = 3$

Assignment
ECT2036: CIRCUITS AND SIGNALS

For $s = 0$: $5 = A + 2B + 4C$; $5 = 3 + 2B + 4(1)$; $B = -1$

$$F(s) = \frac{3}{(s+2)^2} - \frac{1}{(s+2)} + \frac{1}{(s+1)}$$

$$\begin{aligned} F(t) &= 3L^{-1}\left[\frac{1}{(s+2)^2}\right] - L^{-1}\left[\frac{1}{(s+2)}\right] + L^{-1}\left[\frac{1}{(s+1)}\right] \\ &= 3te^{-2t} - e^{-2t} + e^{-t} \\ &= (3t-1)e^{-2t} + e^{-t} \end{aligned}$$

(ii) $F(s) = \frac{10(s+1)}{s(s^2+6s+10)}$

By using method of convolution:

$$F(s) = F_1(s) + F_2(s)$$

$$\begin{aligned} \frac{10(s+1)}{s(s^2+6s+10)} &= \left(\frac{10}{s}\right)\left(\frac{s+1}{s^2+6s+10}\right) \\ &= \left(\frac{10}{s}\right)\left(\frac{s+1}{(s+3)^2+1}\right) \end{aligned}$$

$$F_1(t) = 10L^{-1}\left(\frac{1}{s}\right) = 10u(t)$$

$$F_2(s) = \frac{s+1}{(s+3)^2+1} = \frac{s+1}{(s+3+j)(s+3-j)}$$

From partial fraction, we get:

$$\begin{aligned} \frac{s+1}{(s+3+j)(s+3-j)} &= \frac{A_C}{s+3+j} + \frac{A_C^*}{s+3-j} \\ \frac{s+1}{(s+3-j)} &= \frac{A_C}{s+3+j} \\ A_C &= \left. \frac{s+1}{(s+3-j)} \right|_{s=-3-j} \\ &= \frac{-2-j}{-2j} \end{aligned}$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

$$= \frac{2+j}{2j} \cdot \frac{j}{j}$$

$$= 1 - j$$

$$A_C = \sqrt{1^2 + (-1)^2} \angle \tan^{-1}(-1/1)$$

$$= 1.414 \angle -45^\circ$$

To find A_C^* , the complex conjugate of A_C :

$$A_C^* = 1 + j$$

$$A_C^* = \sqrt{1^2 + 1^2} \angle \tan^{-1}(1/1)$$

$$= 1.414 \angle 45^\circ$$

$$F_2(s) = \frac{1.414 \angle -45^\circ}{s+3+j} + \frac{1.414 \angle 45^\circ}{s+3-j}$$

$$F_2(t) = L^{-1}[F(s)]$$

$$= 2|1.414|e^{-3t} \cos(t+45^\circ)$$

$$= 2.828e^{-3t} \cos(t+45^\circ)$$

$$(iii) \quad F(s) = \frac{se^{-4s}}{(s+2)(s+3)}$$

By using partial fraction:

$$\begin{aligned} \frac{se^{-4s}}{(s+2)(s+3)} &= \left(\frac{A}{s+2} + \frac{B}{s+3} \right) e^{-4s} \\ &= \left(\frac{A(s+3) + B(s+2)}{(s+2)(s+3)} \right) e^{-4s} \end{aligned}$$

$$\Rightarrow se^{-4s} = (A(s+3) + B(s+2))e^{-4s}$$

$$\text{For } s = -2: \quad -2e^{-4s} = Ae^{-4s}; \quad A = -2$$

$$\text{For } s = -3: \quad -3e^{-4s} = -Be^{-4s}; \quad B = 3$$

$$F(s) = \left(\frac{3}{s+3} - \frac{2}{s+2} \right) e^{-4s}$$

$$F(t) = \left(3L^{-1}\left[\frac{1}{s+3}\right] - 2L^{-1}\left[\frac{1}{s+2}\right] \right) L^{-1}[e^{-4s}]$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

$$= (3e^{-3t} - 2e^{-2t})tu(t) \Big|_{t=t-4}$$

$$= (3e^{-3(t-4)} - 2e^{-2(t-4)})[(t-4)u(t-4)]$$

- b) In the network of Figure Q4b, the switch is moved from position 1 to position 2 at time $t = 0$. Just before the switch is moved to position 2, the initial conditions are: $i_L(0^-) = 1A$, $v_C(0^-) = 3V$. Using frequency analysis, find the current $i(t)$ for $t > 0$.

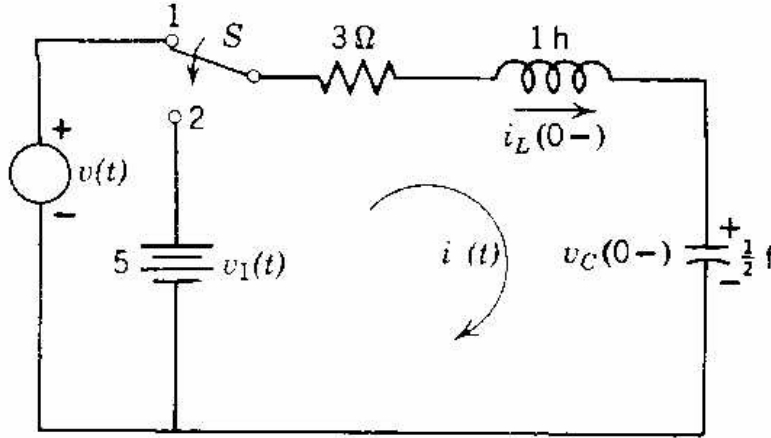


Figure Q4b

Since switch is at position 1 for a long time, capacitor is fully charged.

Given $v_C(0^-) = 3V \rightarrow v(t) = 3V$

Take KVL for voltage equation across the loop:
(Integro-differential equation at $t = 0^-$)

$$V_{dc} = V_R + V_L + V_C$$

$$= Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

$$3 = 3i(t) + 1 \frac{di(t)}{dt} + \frac{1}{(1/2)} \int i(t) dt$$

$$3 = 3i(t) + \frac{di(t)}{dt} + 2 \int i(t) dt$$

To find current $i(t)$ for $t > 0$, take Laplace transform for each voltage element in the loop.

$$V(t) = v_1(t) \rightarrow V(s) = \frac{v_1(t)}{s} = \frac{5}{s}$$

$$V(t) = R \cdot i(t) \rightarrow V(s) = R \cdot I(s) = 3I(s)$$

$$V(t) = L \cdot \frac{di(t)}{dt} \rightarrow V(s) = Ls \cdot I(s) = 1s \cdot I(s)$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

$$V(t) = \frac{1}{C} \int i(t) dt \rightarrow V(s) = \frac{I(s)}{Cs} = \frac{1}{(1/2)s} I(s) = \frac{2}{s} I(s)$$

Current flowing across elements in the loop:

$$3I(s) + sI(s) + \frac{2}{s} I(s) + \frac{5}{s} = 0$$

$$I(s) \left(3 + s + \frac{2}{s} \right) = -\frac{5}{s}$$

$$I(s) = -\frac{5}{s \left(3 + s + \frac{2}{s} \right)} = -\frac{5}{s^2 + 3s + 1}$$

Make it into the form of

$$I(s) = \frac{\omega_0^2}{s^2 + 2\xi\omega_0 s + \omega_0^2} = -\frac{5}{s^2 + 3s + 1}$$

From the quadratic equation: $s^2 + 3s + 1$

$$\begin{aligned} s &= \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \\ &= \frac{-3 \pm \sqrt{3^2 - 4(1)(1)}}{2(1)} \\ &= \frac{-3 \pm \sqrt{5}}{2} \end{aligned}$$

$$I(s) = -5 \left[\left(s + \frac{3 + \sqrt{5}}{2} \right) \left(s + \frac{3 - \sqrt{5}}{2} \right) \right]^{-1}$$

Perform partial fraction decomposition:

$$\begin{aligned} \Rightarrow \frac{1}{\left(s + \frac{3 + \sqrt{5}}{2} \right) \left(s + \frac{3 - \sqrt{5}}{2} \right)} &= \frac{A}{s + \frac{3 + \sqrt{5}}{2}} + \frac{B}{s + \frac{3 - \sqrt{5}}{2}} \\ &= \frac{A \left(s + \frac{3 - \sqrt{5}}{2} \right) + B \left(s + \frac{3 + \sqrt{5}}{2} \right)}{\left(s + \frac{3 + \sqrt{5}}{2} \right) \left(s + \frac{3 - \sqrt{5}}{2} \right)} \end{aligned}$$

$$\Rightarrow 1 = A \left(s + \frac{3 - \sqrt{5}}{2} \right) + B \left(s + \frac{3 + \sqrt{5}}{2} \right)$$

$$\text{For } s = -\frac{3 - \sqrt{5}}{2} :$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

$$\Rightarrow 1 = A \left(s + \frac{3-\sqrt{5}}{2} \right) \Rightarrow A = \frac{1}{\left(-\frac{3-\sqrt{5}}{2} + \frac{3-\sqrt{5}}{2} \right)} = -\sqrt{5}$$

For $s = -\frac{3+\sqrt{5}}{2}$:

$$\Rightarrow 1 = B \left(s + \frac{3+\sqrt{5}}{2} \right) \Rightarrow B = \frac{1}{\left(-\frac{3+\sqrt{5}}{2} + \frac{3+\sqrt{5}}{2} \right)} = \sqrt{5}$$

$$I(s) = \frac{5\sqrt{5}}{s + \frac{3+\sqrt{5}}{2}} - \frac{5\sqrt{5}}{s + \frac{3-\sqrt{5}}{2}}$$

$$I(s) = (5\sqrt{5}) \cdot \left(\frac{1}{s + \frac{3+\sqrt{5}}{2}} - \frac{1}{s + \frac{3-\sqrt{5}}{2}} \right)$$


Take inverse Laplace transform to obtain t-domain function:

$$I(t) = L^{-1}[I(s)]$$

$$I(t) = (5\sqrt{5}) \cdot \left(L^{-1} \left[\frac{1}{s + \frac{3+\sqrt{5}}{2}} \right] - L^{-1} \left[\frac{1}{s + \frac{3-\sqrt{5}}{2}} \right] \right)$$

$$I(t) = (5\sqrt{5}) \cdot \left(e^{\frac{3+\sqrt{5}}{2}t} - e^{\frac{3-\sqrt{5}}{2}t} \right)$$

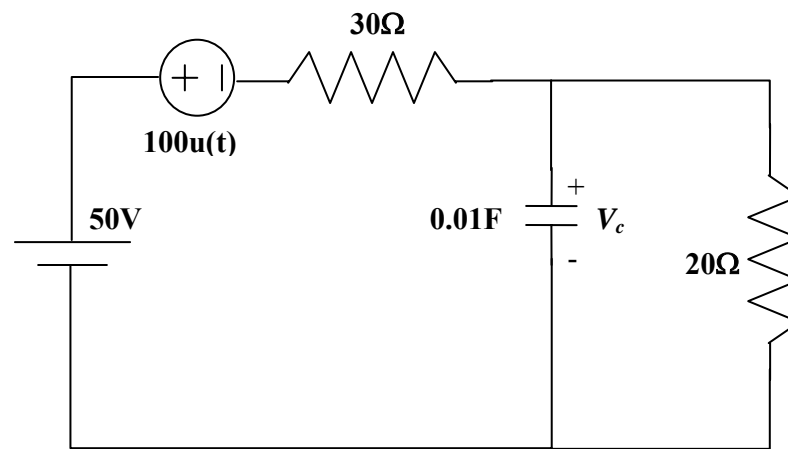- c) For the network given in Figure Q4c; calculate the voltage across capacitor, V_c .



Assignment
ECT2036: CIRCUITS AND SIGNALS

Figure Q4c

Question 5

- a) Derive the ABCD parameters in terms of impedances Z_1 , Z_2 and Z_3 for each of the network given in Figures Q5a and Q5b respectively.

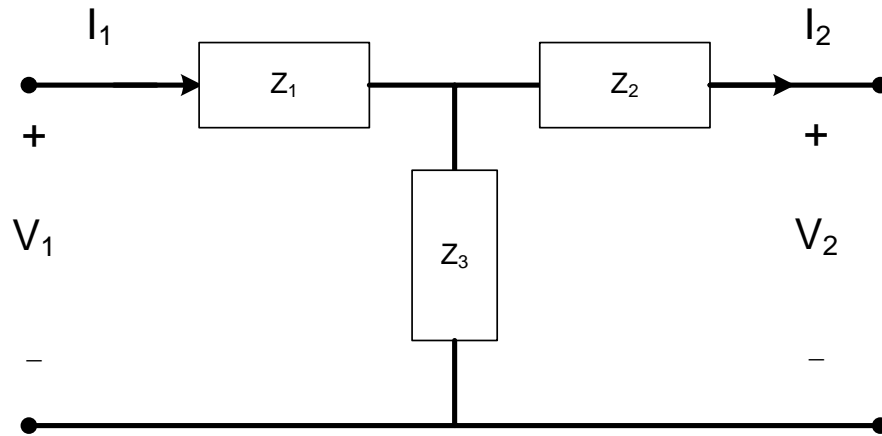


Figure Q5a: T-network

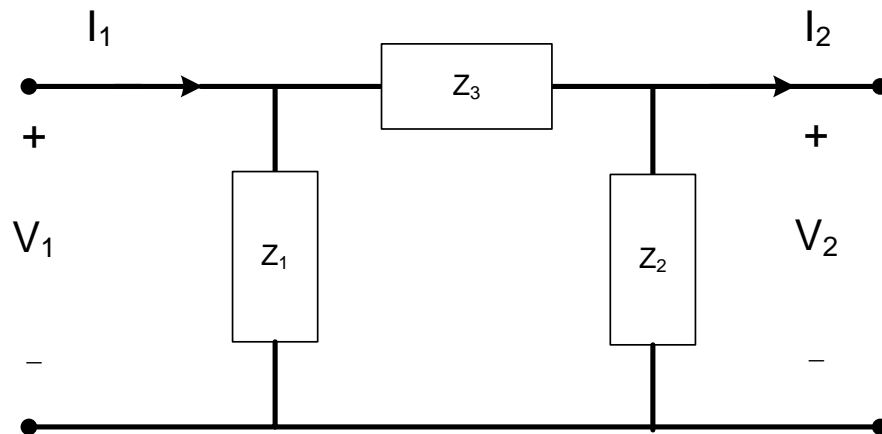


Figure 5b: Π-network

- b) Given:
- i) Z_1 is an impedance for a 10Ω resistor,
 - ii) Z_2 is an impedance for an inductor with inductance of $8\mu\text{H}$
 - iii) Z_3 is an impedance for a capacitor with capacitance of 4 nF

Find the values for each of the ABCD parameters.

Assignment
ECT2036: CIRCUITS AND SIGNALS

For T-network:

Take Z-parameter equation:

$$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$V_1 = I_1(Z_1 + Z_3) + I_2 Z_3$$

$$V_2 = I_1 Z_3 + I_2(Z_2 + Z_3)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 & I_2 \end{bmatrix} \cdot \begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix}$$

$$Z_1 + Z_3 = Z_{11} \Rightarrow Z_1 = Z_{11} - Z_{12} \Rightarrow 10\Omega$$

$$Z_3 = Z_{12} = Z_{21} \Rightarrow Z_2 = Z_{22} - Z_{12} \Rightarrow 8\mu H$$

$$Z_2 + Z_3 = Z_{21} \Rightarrow Z_3 = Z_{12} = Z_{21} \Rightarrow 4nF$$

Transform Z-parameter into ABCD (t-parameter):

By using formula given in lecture notes:

$$\begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta z}{z_{21}} \\ 1 & \frac{z_{22}}{z_{21}} \end{bmatrix}$$

Where $\Delta z = z_{11}z_{22} - z_{21}z_{12}$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{z_1 + z_3}{z_3} & \frac{(z_1 + z_3)(z_2 + z_3) - z_3^2}{z_3} \\ 1 & \frac{z_2 + z_3}{z_3} \end{bmatrix}$$

$$A = \frac{10 - j4 \times 10^{-9}}{-j4 \times 10^{-9}} = 1 + j2.5 \times 10^9 \Omega$$

$$B = \frac{(10 - j4 \times 10^{-9})(j8 \times 10^{-6} - j4 \times 10^{-9}) - (-j4 \times 10^{-9})^2}{-j4 \times 10^{-9}} = -19990 + j8 \times 10^6 \Omega$$

$$C = \frac{1}{-j4 \times 10^{-9}} = j2.5 \times 10^9 \Omega$$

$$D = \frac{j8 \times 10^{-6} - j4 \times 10^{-9}}{-j4 \times 10^{-9}} = 1999 \Omega$$

Please note that for ABCD parameters calculations, intermediate steps involve to obtain final value are not shown in full.

Assignment
ECT2036: CIRCUITS AND SIGNALS

For π -network:

Take Y-parameter equation:

$$Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_A + Y_B$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -Y_B$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -Y_B$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_B + Y_C$$

$$Y_A = Y_{11} + Y_{12} = Z_1^{-1} = 1/Z_1$$

$$Y_B = -Y_{12} = -Y_{21} = Z_3^{-1} = 1/Z_3$$

$$Y_C = Y_{22} + Y_{21} = Z_2^{-1} = 1/Z_2$$

Transform Y-parameter into ABCD (t-parameter):

By using formula given in lecture notes:

$$\begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-\Delta y}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix}$$

Where $\Delta y = y_{11}y_{22} - y_{21}y_{12}$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{Y_B + Y_C}{Y_B} & \frac{1}{Y_B} \\ \frac{Y_A + Y_B + Y_B^2}{Y_B} & \frac{Y_A + Y_B}{Y_B} \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{z_3}{z_2} & z_3 \\ 1 + \frac{z_3}{z_1} + \frac{1}{z_3} & 1 + \frac{z_3}{z_1} \end{bmatrix}$$

$$A = 10 - \frac{j4 \times 10^{-9}}{j8 \times 10^{-6}} = 9.9995\Omega$$

Assignment
ECT2036: CIRCUITS AND SIGNALS

$$B = -j4 \times 10^{-9} \Omega$$

$$C = 1 - \frac{j4 \times 10^{-9}}{10} + \frac{1}{j4 \times 10^{-9}} = -j4 \times 10^{-10} \Omega$$

$$D = 1 - \frac{j4 \times 10^{-9}}{10} = 1 - j4 \times 10^{-10} \Omega$$

Please note that for ABCD parameters calculations, intermediate steps involve to obtain final value are not shown in full.

END OF SOLUTION

Enjoy your day.

Solution prepared by Uncle Lim.
Wednesday, September 06, 2006

Revised Monday, September 11, 2006
Version 2 uploaded Monday, September 11, 2006

Credits:

Thank to Old Son (Lao Zhi), Ray, Wilson for their contribution on error checking.

Here is some information regarding Uncle Lim, in which you might have some interests to know about. Uncle Lim generally refers to a person that's referring back to himself, translated from the context of Chinese terminology "Lim Pek". In English terms, we can refer this to "me", the person who prepared this document. When that person says, I wrote this solution, the word I refer to Uncle Lim as well. Uncle Lim basically means me, myself, or I, when you are about to mention something to another person from your point of view, originally used for those who wish to say something that refers back to his own. In the context of this document, Uncle Lim means "Lim Pek", and again, the person who developed the answer to the question, but not those who copies the solution prepared by Uncle Lim.

Disclaimer: Use this document at your own responsibility. Do not assume answers given are correct and error-free. Uncle Lim holds no responsibility in the event that answers or copies submitted contain mistakes that are exact or identical. This is not a copyrighted or intellectually protected material. Information provided is only a person's effort to solve the problems at its own ability. It is not encouraged to make free distribution, duplication or circulation of this document in any form, either manually or electronically.