

- Consider the circuit sketched in Figure 4.7, what is the magnitude and direction of electric current .
(Answer : $0.5A$, counterclockwise)

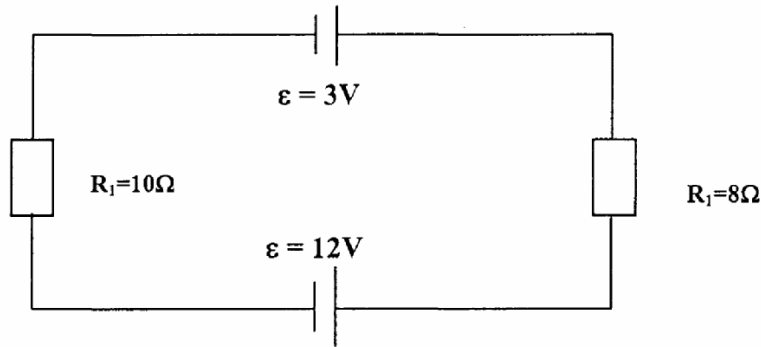


Figure 4.7

- Find the current in the circuit shown in Figure 4.8

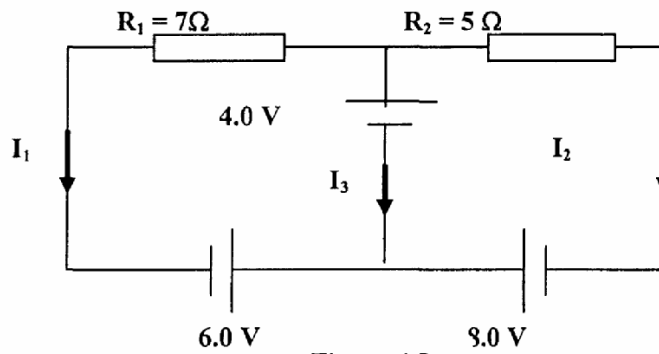


Figure 4.8

(Answer : $I_1 = 1.43A$, $I_2 = 2.4 A$, $I_3 = - 3.8A$)

- From the figure 4.9 find
 - I_1 , I_2 and I_3
 - Potential at point F if point B was grounded.

(Answer : $-1.7A$, $2.1A$, $-0.4A$, $+8.4V$)

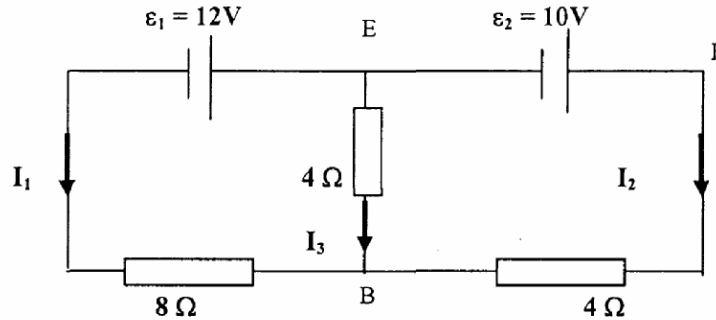


Figure 4.9

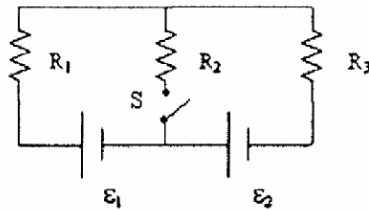


Figure 4.10

- 4 a) In the figure 4.10, if the current through R_1 is 5 A up and if the current through R_3 is 3 A up, what is the current in R_2 if the switch S is closed?
 - b) If $R_1 = 6\ \Omega$, $R_2 = 8\ \Omega$, $R_3 = 2\ \Omega$, $\varepsilon_1 = 4\text{ V}$, and $\varepsilon_2 = 14\text{ V}$ and the switch S is closed
 - i) what is the current in R_2 ?
 - ii) Find the voltage drops across the resistors in the circuit?
 - iii) what is the power supplied to the circuit by ε_1 ?
 - c) If $R_1 = 6.0\ \Omega$, $R_2 = 8.0\ \Omega$, $R_3 = 2.0\ \Omega$, $\varepsilon_1 = 4.0\text{ V}$, and $\varepsilon_2 = 14\text{ V}$, what is the current flows in the circuit if S is open?
- (Answer a) 8 A, b) i) 1A, ii) $V_1 = 12V$, $V_2 = 8\text{ V}$, $V_3 = 6V$ c) $28/8\text{ A}$)
5. What shunt resistance should be connected in parallel with an ammeter having a resistance of $0.04\ \Omega$ so that 25 percent of the total current will pass through the ammeter.
(Answer : $0.013\ \Omega$)
 6. A $36\ \Omega$ galvanometer is shunted by a resistor of $4.0\ \Omega$. What part of the total current will pass through the instrument?
(Answer : $1/10$)
 7. A relay having a resistance of $6\ \Omega$ operates with a minimum current of 0.03 A . It is required that the relay operate when acurrent in the line reaches 0.24 A . What resistance should be used to shunt the relay?
(Answer : $0.86\ \Omega$)