

THE HONG KONG POLYTECHNIC UNIVERSITY
FACULTY OF ENGINEERING

Programmes : BEng(Hons)/MEng in Mechanical Engineering
BEng(Hons)/MEng in Industrial and Systems Engineering

Programme Codes : 43078, 45085

Subject Title : Basic Electricity & Electronics **Subject Code** : ENG233

Session : Semester 1, 2003/2004

Date : 17 December 2003 **Time** : 09:30-12:30

Time Allowed : 3 hours **Subject Examiner(s)** : Prof. D. Sutanto(EE)
Dr David Cheng(EIE)

This question paper has a total of 11 pages (attachments included).

Instructions to Candidates :

This is an open-book examination. Candidates are allowed to bring in the following text book:
“G. Rizzoni, Principles and Applications of Electrical Engineering, McGraw-Hill Higher Education.”

Answer ALL multiple choice questions in Section A (40 marks) by circling the correct answer in the exam paper AND answer ALL Questions in Section B (60 marks).

Physical Constants :

Other Attachments :

Available from Invigilator : Graph Paper

DO NOT TURN OVER THE PAGE UNTIL YOU ARE TOLD TO DO SO.

SECTION B: Answer ALL FOUR Questions. It is advisable to show all your working for section B as marks will be awarded for partial answers.

QUESTION 1

Consider the circuit shown in Figure Q1.

Resistors R1 and R2 = 1 kΩ, while R3, R4, R5, R6 and R7 are 2 kΩ:

Batteries, V1 and V2= 10V while V3 = 12V

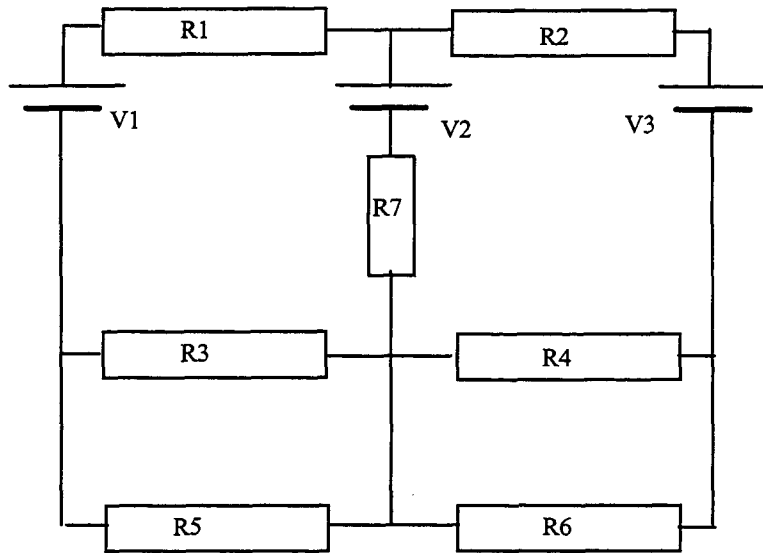


Figure Q1

- (a) Redraw and simplify the circuit as much as possible into your exam booklet showing appropriate current loops and the current that flows in each resistor. (4 marks)
- (b) Write down sufficient equations which will enable you to calculate the currents through all the batteries. (7 marks)
- (c) Calculate the currents through all 3 of the batteries. (4 marks)

QUESTION 2

The circuits in Figure Q2 show simplified diagrams of an automobile spark-coil circuit. The spark gap is a break in the circuit that allows a spark to jump (i.e. a current to conduct) when the voltage gets high enough.

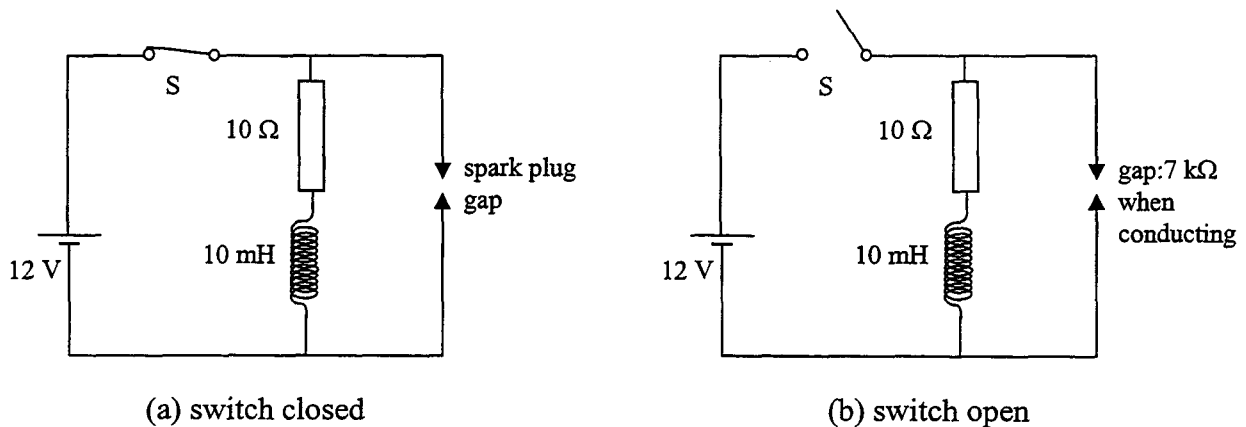


Figure Q2

Semester 1, 2003/04

Subject Code: ENG233

A rotor synchronised with the engine closes the switch S , for a long enough time that a sufficiently large current builds up in the inductor.

- (a) On the graph paper provided, sketch a graph of the current in the circuit (through the switch) when the switch is closed. Indicate on the graph the value of the steady state current. (4 marks)
- (b) Estimate the time for which the switch must remain in contact in order for the current to build up to about 1 A. (5 marks)

When the switch opens, the interruption of the current causes a large induced emf to develop across the inductor and hence the spark gap, causing a spark (i.e. a current) to jump the gap. As the spark current decreases so does the emf and the sparking stops. When conducting, the effective resistance of the spark gap is about $7\text{ k}\Omega$.

- (c) Estimate the duration of the spark current. (3 marks)
- (d) Estimate the voltage generated across the spark gap. (3 marks)

QUESTION 3

The circuit shown in Figure Q3 is a 4-bit digital-to-analogue converter (DAC). Each switch is controlled by the corresponding bit of the digital number. If the bit is 1, the switch is connected to -5 V ; if the bit is 0, the switch is connected to 0 V . Let the digital number be represented by $b_3b_2b_1b_0$.

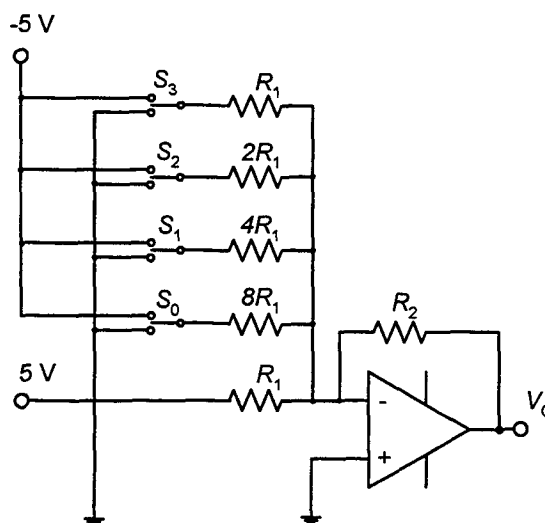


Figure Q3

- (a) Determine an expression relating the output V_O to the binary input bits. (4 marks)
- (b) If $R_2=2\text{ k}\Omega$ and $R_1=1.25\text{ k}\Omega$, find the output voltage V_O if $b_3b_2b_1b_0 = 1100$. (3 marks)
- (c) What is the resolution over the range of V_O from -8 V to 7 V ? (4 marks)
- (d) Find the number of bits required in the DAC if an improved resolution of 0.5 V is desired. (4 marks)

QUESTION 4

An RC coupled common-emitter amplifier is shown in Figure Q4 with:

- $C_S = 2.2 \mu\text{F}$, $C_C = 0.47 \mu\text{F}$, $C_E = 20 \mu\text{F}$,
- $R_1 = 30 \text{ k}\Omega$, $R_2 = 5.6 \text{ k}\Omega$, $R_C = 4.7 \text{ k}\Omega$, $R_E = 1.5 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$, $R_S = 200 \Omega$,
- $V_{CC} = 20 \text{ V}$, $\beta = 100$,

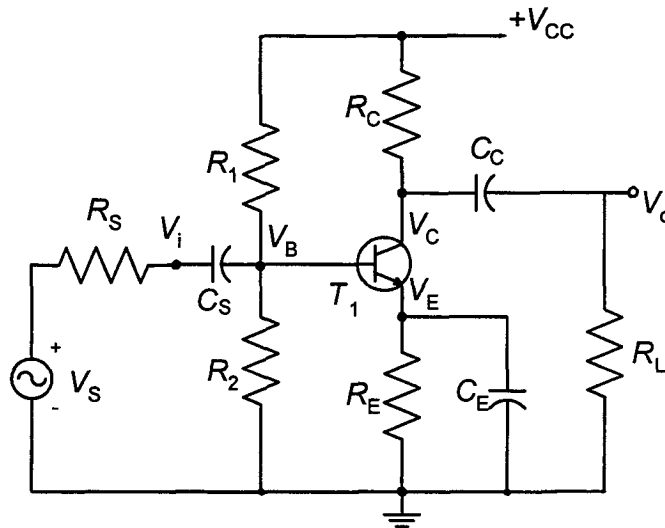


Figure Q4

- (a) Calculate I_{BQ} , I_{CQ} , and V_{CEQ} . (The dc operating point for the transistor T_1 .) (9 marks)
- (b) Determine the region of operation of the transistor T_1 . (3 marks)
- (c) If the resistor R_L is short-circuited, what will happen to the voltage V_{CEQ} ? (3 marks)